

**UGC NET PAPER 3 JANUARY 03, 2017 SHIFT 1 ELECTRONIC SCIENCE QUESTION PAPER**

**Note :** This paper contains **seventy five (75)** objective type questions of **two (2)** marks each. All questions are compulsory.


1. A conducting line on an IC chip is 2.8 mm long and has a rectangular cross-section of  $1 \mu\text{m} \times 4 \mu\text{m}$ . A current of 5 mA produces a voltage drop of 100 mV across the line. If the electron mobility is  $500 \text{ cm}^2/\text{V-s}$ , the electron concentration is

- (1)  $4.38 \times 10^{21} \text{ cm}^{-3}$  (2)  $3.5 \times 10^{17} \text{ cm}^{-3}$   
 (3)  $5.48 \times 10^{21} \text{ cm}^{-3}$  (4)  $4.6 \times 10^{20} \text{ cm}^{-3}$

2. In a MOSFET the drain saturation current is


- (1)  $\frac{\mu_n C_{ox} W}{L} (V_{gs} - V_{th})$   
 (2)  $\frac{\mu_n C_{ox} W}{2L} (V_{gs} - V_{th})^2$   
 (3)  $\frac{\mu_n C_{ox} W}{2L} (V_{gs} - V_{th}) v_{ds}$   
 (4)  $\frac{\mu_n C_{ox} L}{W} (V_{gs} - V_{th})^2$

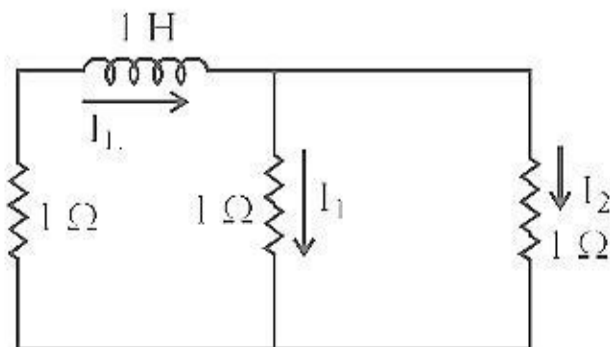3. The time constant for the network shown below will be :



- (1)  $\frac{1}{3} \text{ sec}$  (2)  $\frac{2}{3} \text{ sec}$   
 (3) 1 sec (4) 3 sec

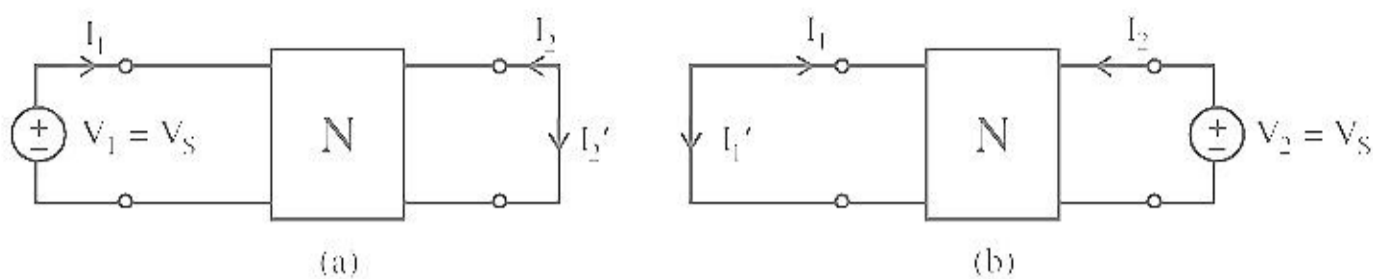
4. Consider the networks shown in the following figures (a) and (b) :



The above networks are :

- (1) Thevenin's equivalent of each other
- (2) Dual network of each other
- (3) Reciprocal network of each other
- (4) They are symmetrical to each other

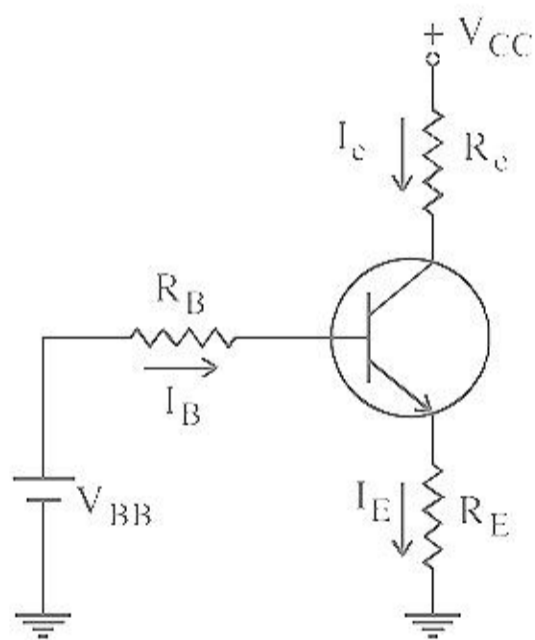5. In a circuit given below the base current  $I_B$  is



- (1)  $\frac{V_{BB}}{R_B}$
- (2)  $\frac{V_{BB} - V_{BE}}{R_B + R_E}$
- (3)  $\frac{V_{BB} - V_{BE}}{R_B + (\beta + 1) R_E}$
- (4)  $\frac{V_{BB}}{R_B + (\beta + 1) R_E}$

6. In a class A large signal amplifier with  $R_L$  as a load resistance,  $I_m$  and  $V_m$  represents the peak sinusoidal current and voltage, the output power is

- (1)  $\frac{(V_{\max} - V_{\min})(I_{\max} - I_{\min})}{2\sqrt{2}}$
- (2)  $\frac{(V_{\max} - V_{\min})(I_{\max} - I_{\min})}{8}$
- (3)  $\frac{V_m \cdot I_m}{\sqrt{2}}$
- (4)  $\frac{(V_{\max} - V_{\min})(I_{\max} - I_{\min})}{2}$

7. In a 4 bit ripple counter and a 4 bit synchronous counter are made using flip-flops having a propagation delay of 10 ns each. If the worst case delay in the ripple counter and the synchronous counter be 'R' & 'S' respectively, then the value of 'R' & 'S' is given by :
- (1)  $R = 10 \text{ ns}, S = 40 \text{ ns}$                       (2)  $R = 40 \text{ ns}, S = 10 \text{ ns}$   
(3)  $R = 10 \text{ ns}, S = 30 \text{ ns}$                       (4)  $R = 30 \text{ ns}, S = 10 \text{ ns}$
8. The Boolean expression  $AC + B\bar{C}$  is equivalent to :
- (1)  $\bar{A}C + B\bar{C} + AC$                       (2)  $\bar{B}C + AC + B\bar{C} + \bar{A}C\bar{B}$   
(3)  $AC + B\bar{C} + \bar{B}C + ABC$                       (4)  $ABC + \bar{A}B\bar{C} + AB\bar{C} + A\bar{B}C$
9. For pushing of flags and popping of flags in 8086, the instructions are :
- (1) Push and Pop                      (2) Push F and Pop F  
(3) Push and Pop F                      (4) None of the above
10. Consider the following set of 8085 instructions :
- ```
MVI A, 8EH  
ADI 73H  
JC DSPLY  
OUT PORT1  
HLT  
DSPLY: XR A  
OUT PORT1  
HLT
```
- The output at PORT1 is :
- (1) FEH                      (2) 01H  
(3) 00                      (4) 11H
11. Which of the following cannot be a member of a structure in 'C' ?
- (1) Enumeration                      (2) Another structure  
(3) Function                      (4) Array




18. A channel with bit rate  $R_b = 36$  Kbps is available for PCM voice transmission. Find the sampling rate  $f_s$ , assuming  $f_m = 3.2$  kHz.

- (1) 7.2 MHz (2) 3.6 MHz  
(3) 3.6 kHz (4) 7.2 kHz

19. The fundamental law that is used in temperature measurement is known as

- (1) First law of thermodynamics (2) Second law of thermodynamics  
(3) Third law of thermodynamics (4) Zeroth law of thermodynamics

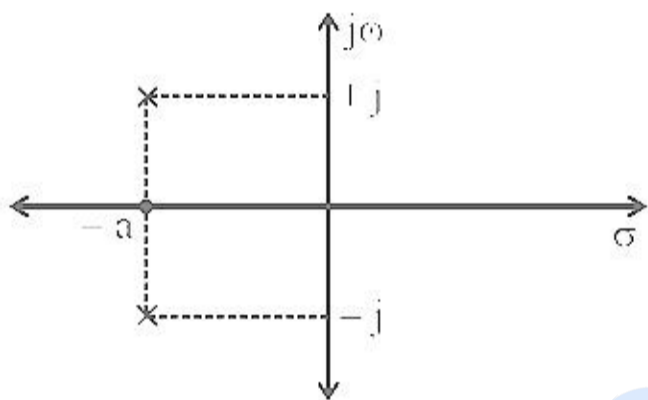20. The location of closed loop poles of a LTI system is given as shown in the figure :



The system will be

- (1) Unstable (2) Marginally stable  
(3) Absolutely stable (4) Relatively stable

21. For non-degenerate semiconductors the product of the majority and minority carrier concentration is fixed as

- (a)  $n_i^2$  (b)  $N_c N_v \exp\left(\frac{E_g}{kT}\right)$   
(c)  $N_c N_v \exp\left(-\frac{E_g}{kT}\right)$  (d)  $N_v \exp\left(-\frac{E_g}{kT}\right)$


Which of the above are correct ?

- (1) (a) and (c) are correct. (2) (b) and (a) are correct.  
(3) (b) is correct, but (a) is wrong. (4) (a) and (d) are correct.

22. In a BJT the collector current in common emitter configuration is

- (1)  $\alpha I_E + I_{CBO}$  (2)  $\alpha I_E + I_{CEO}$   
(3)  $\beta I_B + I_{CBO}$  (4)  $\beta I_B + I_{CEO}$

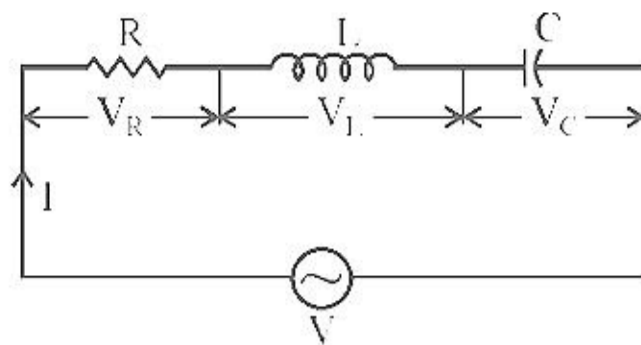23. Consider the following RLC circuit and read the statements given below :



- (a) The current  $I$  is in phase with  $V_R$ .
- (b) The current  $I$  leads  $V_C$  by  $\pi/2$ .
- (c) The current  $I$  lags behind  $V_L$  by  $\pi/2$ .
- (d) The current  $I$  leads  $V_L$  by  $\pi/2$ .

Which of the above statements are correct ?

- (1) Only (a) and (b) are correct.
- (2) Only (b) and (c) are correct.
- (3) Only (a), (b) and (d) are correct.
- (4) Only (a), (b) and (c) are correct.

24. In a common emitter transistor amplifier the current gain can be expressed as

- (a)  $\frac{-h_{fc}}{h_{oc}}$
- (b)  $\frac{-h_{fc}}{1 + h_{oc} R_L}$
- (c)  $\frac{h_{fc}}{1 - h_{oc} R_L}$
- (d)  $\frac{-h_{fc}}{1 - h_{oc} R_L}$

**Options :**

- (1) (a) is correct, but (b) is wrong.
- (2) (b) and (d) are correct.
- (3) (b) is correct, but (d) is wrong.
- (4) (c) and (d) are correct.

25. Read the following statements regarding complexity of a network :

- (a) The order of complexity of a network is defined as the number of independent initial conditions that can be specified in a network.
- (b) The number of state equations that can be written for a network is equal to the order of the complexity of the network.
- (c) The order of complexity is always more than the number of energy storing elements.
- (d) The number of state equations that can be written for a network is always higher than the number of energy storing elements.

Which of the above statements are correct ?

- (1) (a) and (b) are correct.
- (2) (b) and (c) are correct.
- (3) (c) and (d) are correct.
- (4) (a) and (c) are correct.



29. Consider the following registers :

- |                       |                       |
|-----------------------|-----------------------|
| (a) A and B registers | (b) B and C registers |
| (c) D and E registers | (d) H and L registers |

Which of these 8-bit registers of 8085 microprocessor can be paired together to make a 16 bit register ?

- |                      |                      |
|----------------------|----------------------|
| (1) (a), (c) and (d) | (2) (a), (b) and (c) |
| (3) (b), (c) and (d) | (4) (b), (d) and (a) |

30. Consider the following instructions of 8085 microprocessor :

- |               |           |
|---------------|-----------|
| (a) MOV M, A  | (b) ADD C |
| (c) MVI A, FF | (d) CMP M |

Which of these cause change in the status of flag(s) ?

- |                 |                 |
|-----------------|-----------------|
| (1) (a) and (b) | (2) (b) and (d) |
| (3) (a) and (c) | (4) (b) and (c) |

31. Which of the following functions manipulate the value of file position indicator ?

- |               |                |
|---------------|----------------|
| (a) ftell( )  | (b) fgetpos( ) |
| (c) rewind( ) | (d) fgetc( )   |

**Codes :**

- |                                   |                                        |
|-----------------------------------|----------------------------------------|
| (1) (a) and (b) are correct.      | (2) (c) and (d) are correct.           |
| (3) (a), (b) and (c) are correct. | (4) (a), (b), (c) and (d) are correct. |

32. Which of the following statements are correct about the C declarations given below ?

```
char *p = "Honesty";
```

```
char a[ ] = "Honesty";
```

- |                                                                                                                               |
|-------------------------------------------------------------------------------------------------------------------------------|
| (a) There is no difference in the declarations and both serve the same purpose.                                               |
| (b) In both cases the '\0' will be added at the end of the string "Honesty".                                                  |
| (c) The first statement is incorrect since '\0' is not given in the string.                                                   |
| (d) 'p' is a non-const pointer pointing to a non-const string, whereas 'a' is a const pointer pointing to a non-const string. |

**Codes :**

- |                              |                              |
|------------------------------|------------------------------|
| (1) (a) and (b) are correct. | (2) (c) and (d) are correct. |
| (3) (a) and (c) are correct. | (4) (b) and (d) are correct. |





36. Which of the following statements are correct ?

- (a) In CDMA, the entire bandwidth can be used all the time.
- (b) TDMA is a technique which does not allow for spectrum re-use i.e. utilizing same spectrum in different time slots.
- (c) TDMA has primary disadvantage of susceptibility for station cross-linking.
- (d) FDMA is the simplest & most basic format Multiple Access Communications.

**Options :**

- (1) (b) & (c) are correct.
- (2) (a), (c) & (d) are correct.
- (3) (a) & (d) are correct.
- (4) (c) & (d) are correct.

37. Which of the following statements are correct in case of Light Emitting Diodes ?

- (a) Homojunctions LEDs are often surface emitters.
- (b) Heterojunctions LEDs are Edge emitters.
- (c) Heterojunction LEDs are often surface emitters.
- (d) LEDs provide monochromatic & coherent radiations.

**Options :**

- (1) (a) & (b) are correct.
- (2) (a) & (c) are correct.
- (3) (a), (b) & (d) are correct.
- (4) (a), (c) & (d) are correct.

38. Which of the following statements are incorrect in case of semiconductor LASERS ?

- (a) Stimulated emission rate dominates the spontaneous emission with increase in the value of energy of radiation per unit volume per unit frequency.
- (b) Stimulated emission rate dominates the absorption rate of the charge carriers in the ground state are higher than the excited state.
- (c) LASERS have a longer life-time than LEDs.
- (d) LASER diodes are more temperature sensitive than LEDs.

**Options :**

- (1) (c) & (d) are incorrect.
- (2) (a), (c) and (d) are incorrect.
- (3) (a) & (d) are incorrect.
- (4) (b) & (c) are incorrect.

39. Read the following statements regarding biomedical instrumentations :

- (a) Sphygmomanometer is used for blood pressure measurement.
- (b) EMG represents a record of the electrical activity of the brain.
- (c) ERG represents the record of potential from the retina.
- (d) ECG represents the record of electrical activity of brain.

Which of the above statements are correct ?

- (1) (a) and (b) are correct.
- (2) (b) and (c) are correct.
- (3) (a) and (c) are correct.
- (4) (b) and (d) are correct.

40. Read the following statements regarding PID controller :

- (a) The system complexity of a PID controller is less than that of a PI controller.
- (b) A PID controller produces no action for any constant error signal.
- (c) A PID controller is used to increase the damping factor of the dominant poles of a PI controlled system.
- (d) A PID controller is used to decrease the damping factor of the dominant poles of a PI controlled system.

Which of the above statements are correct ?

- (1) (a) and (b)
- (2) (b) and (c)
- (3) (a) and (d)
- (4) (b) and (d)

41. Match the following lists :

**List – I**

- a. Abrupt p-n junction
- b. Linearly graded p-n junction
- c. Tunnel diode
- d. p-i-n diode

**List – II**

- i. 

|       |       |
|-------|-------|
| $p^+$ | $n^+$ |
|-------|-------|
- ii. 

|       |     |       |
|-------|-----|-------|
| $p^+$ | $n$ | $n^+$ |
|-------|-----|-------|
- iii. 

|     |          |     |
|-----|----------|-----|
| $p$ | $\pi(v)$ | $n$ |
|-----|----------|-----|
- iv. 

|       |     |     |       |
|-------|-----|-----|-------|
| $p^+$ | $p$ | $n$ | $n^+$ |
|-------|-----|-----|-------|

Correct codes are :

**Codes :**

- |     | a  | b   | c   | d   |
|-----|----|-----|-----|-----|
| (1) | ii | iv  | i   | iii |
| (2) | i  | ii  | iii | iv  |
| (3) | ii | iii | iv  | i   |
| (4) | iv | i   | ii  | iii |

42. Match the following lists :

**List – I**

**List – II**

- |                                   |                          |
|-----------------------------------|--------------------------|
| a. Negative real and simple roots | i. Sustained oscillatory |
| b. Negative real and equal roots  | ii. Overdamped           |
| c. Complex conjugate roots        | iii. Critically damped   |
| d. Imaginary conjugate roots      | iv. Underdamped          |

Correct codes are :

**Codes :**


- |     | a   | b   | c  | d  |
|-----|-----|-----|----|----|
| (1) | iii | ii  | iv | i  |
| (2) | iii | ii  | i  | iv |
| (3) | ii  | iii | i  | iv |
| (4) | ii  | iii | iv | i  |

43. Match the following lists :


**List – I**

**List – II**


a. Voltage doubler

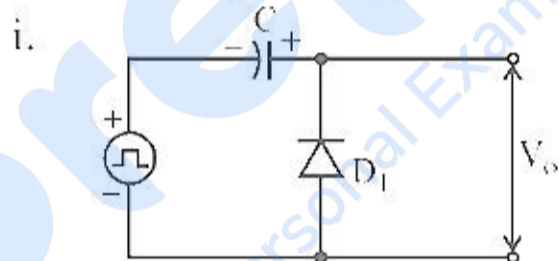


b. Halfwave rectifier

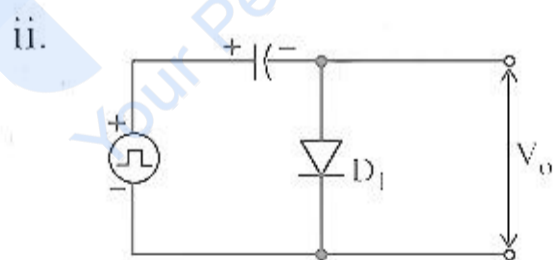

c. Positive clamping circuit

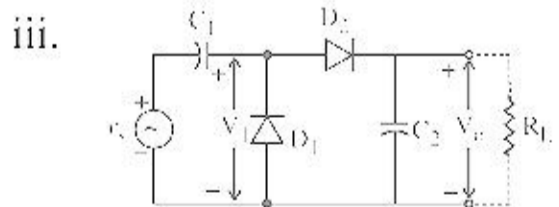

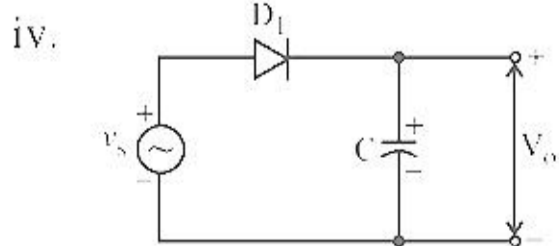

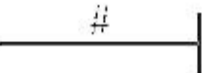

d. Negative clamping circuit



**Codes :**

- |     | a   | b   | c   | d   |
|-----|-----|-----|-----|-----|
| (1) | i   | ii  | iii | iv  |
| (2) | iii | iv  | i   | ii  |
| (3) | ii  | iii | i   | iv  |
| (4) | iv  | i   | ii  | iii |

44. Match the following lists in terms of qualifying symbols for inputs and outputs :

| List – I                                                                             | List – II                        |
|--------------------------------------------------------------------------------------|----------------------------------|
| a.  | i. Non-logic connection          |
| b.  | ii. Input for digital signals    |
| c.  | iii. Logic negation at the input |
| d.  | iv. Active low input             |

Correct codes are :

Codes :

|     | a  | b   | c  | d   |
|-----|----|-----|----|-----|
| (1) | iv | i   | ii | iii |
| (2) | iv | ii  | i  | iii |
| (3) | ii | i   | iv | iii |
| (4) | i  | iii | ii | iv  |

45. Match the following lists in 8085 :

| List – I   | List – II      |
|------------|----------------|
| Interrupt  | Vector Address |
| a. RST 7.5 | i. 0034H       |
| b. RST 6.5 | ii. 0024H      |
| c. RST 5.5 | iii. 003CH     |
| d. TRAP    | iv. 002CH      |

Codes :

|     | a   | b   | c   | d   |
|-----|-----|-----|-----|-----|
| (1) | iv  | ii  | i   | iii |
| (2) | i   | iii | ii  | iv  |
| (3) | ii  | iv  | iii | i   |
| (4) | iii | i   | iv  | ii  |

46. Match the items of List-I in C++ with the items of List-II in FORTRAN :

**List – I**

**List – II**

- |                     |                  |
|---------------------|------------------|
| a. Global variables | i. Computed GOTO |
| b. Static           | ii. EQUIVALENCE  |
| c. Reference        | iii. COMMON      |
| d. Switch           | iv. SAVE         |

**Codes :**

- |     | a   | b   | c   | d   |
|-----|-----|-----|-----|-----|
| (1) | iv  | ii  | i   | iii |
| (2) | ii  | i   | iii | iv  |
| (3) | iii | iv  | ii  | i   |
| (4) | i   | iii | iv  | ii  |

47. Match the following lists :

**List – I**

**List – II**

- |                        |                                  |
|------------------------|----------------------------------|
| a. Beam efficiency     | i. $4\pi/\Omega_A$               |
| b. Directivity         | ii. $kD$                         |
| c. Gain                | iii. $\frac{\Omega_M}{\Omega_A}$ |
| d. Aperture Efficiency | iv. $A_e/A_p$                    |

Correct Codes are :

**Codes :**

- |     | a   | b  | c  | d   |
|-----|-----|----|----|-----|
| (1) | iii | i  | iv | ii  |
| (2) | iv  | i  | ii | iii |
| (3) | iii | i  | ii | iv  |
| (4) | ii  | iv | i  | iii |

48. Match the following lists :

**List – I**

- a. Power efficient transmission of signals
- b. Bandwidth efficient transmission of signals with significant dc signals
- c. Most bandwidth efficient transmission of voice signals
- d. Simplest Receiver Circuit

**List – II**

- i. AM
- ii. VSB
- iii. SSB-SC
- iv. FM

Correct Codes are :

**Codes :**

- |     | a   | b   | c   | d  |
|-----|-----|-----|-----|----|
| (1) | iii | ii  | iv  | i  |
| (2) | ii  | iii | iv  | i  |
| (3) | iii | i   | ii  | iv |
| (4) | iv  | ii  | iii | i  |

49. Match the following lists :

**List – I**

- a. SCR can be turned off by
- b. Turn on time of SCR can be reduced by
- c. Holding current for an SCR means
- d. A forward current can be applied to an SCR after

**List – II**

- i. it turns off when anode current falls below this value.
- ii. the rectangular pulse of high amplitude and narrow width
- iii. its anode current interruption
- iv. its gate recovery time





Correct Codes are :

**Codes :**





- |     | a   | b   | c  | d  |
|-----|-----|-----|----|----|
| (1) | i   | iii | ii | iv |
| (2) | iii | ii  | i  | iv |
| (3) | iii | ii  | iv | i  |
| (4) | i   | iii | iv | ii |

50. Match the following lists :

**List – I**

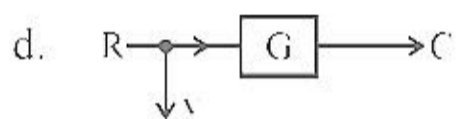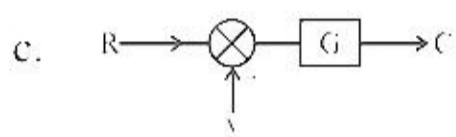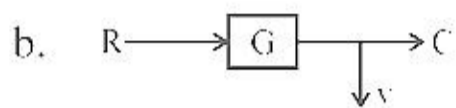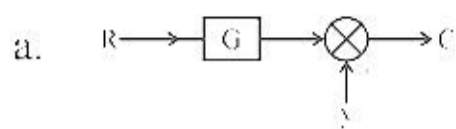

**List – II**

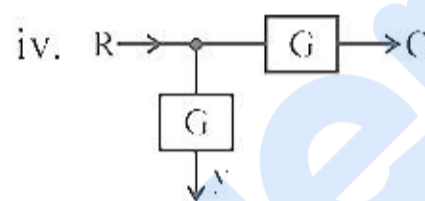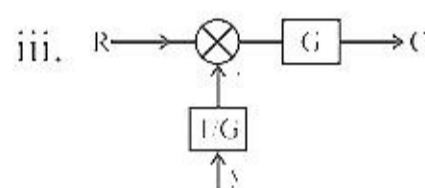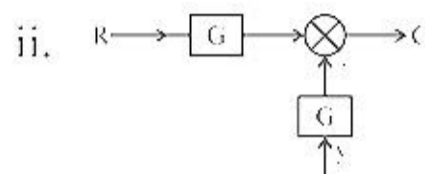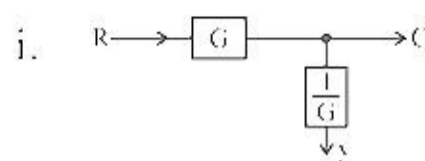

**Codes :**

|     | a   | b   | c  | d   |
|-----|-----|-----|----|-----|
| (1) | ii  | iii | i  | iv  |
| (2) | ii  | i   | iv | iii |
| (3) | iii | iv  | i  | ii  |
| (4) | iii | iv  | ii | i   |

51. Arrange the following materials in ascending order based on their mobility of electrons at 300 K :


- |                      |                     |
|----------------------|---------------------|
| (a) Germanium        | (b) Silicon         |
| (c) Gallium Arsenide | (d) Gallium Nitride |

**Codes :**

|     |     |     |     |     |
|-----|-----|-----|-----|-----|
| (1) | (a) | (b) | (c) | (d) |
| (2) | (b) | (c) | (d) | (a) |
| (3) | (d) | (b) | (a) | (c) |
| (4) | (c) | (d) | (b) | (a) |



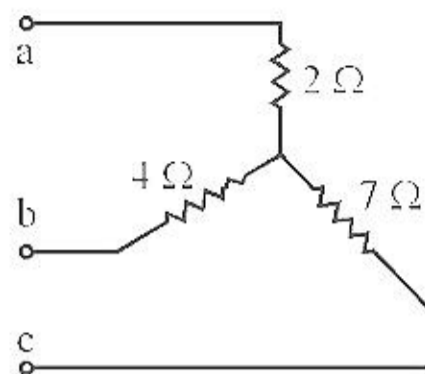52. Consider a star network as shown in the following figure :



If the resistance between terminals b and c with a open is represent by  $R_A$ , the resistance between c and a with b open is  $R_B$  and the resistance between a and b with c open is  $R_C$ , then arrange  $R_A$ ,  $R_B$  and  $R_C$  in descending order.

- (1)  $R_C, R_B, R_A$                       (2)  $R_B, R_C, R_A$   
 (3)  $R_A, R_B, R_C$                       (4)  $R_B, R_A, R_C$

53. Arrange the following fabrication steps in order needed to fabricate the IC :

- (a) Oxidation                              (b) Etching  
 (c) Metallization                        (d) Epitaxial growth

**Codes :**

- (1) (a) (b) (c) (d)  
 (2) (d) (a) (b) (c)  
 (3) (b) (c) (d) (a)  
 (4) (c) (d) (a) (b)

54. For TTL operation in low and high states at the output different voltages are required :

- (a)  $V_{IL, \max}$                               (b)  $V_{IH, \min}$   
 (c)  $V_{OL, \max}$                               (d)  $V_{OIH, \min}$

Arrange the above in ascending order of voltages, the correct code is given by :

**Codes :**

- (1) (c) (a) (b) (d)  
 (2) (b) (a) (c) (d)  
 (3) (a) (b) (c) (d)  
 (4) (d) (b) (a) (c)

55. Arrange the following in descending order w.r.t. their pin numbers of 8251 USART :

- |                             |                             |
|-----------------------------|-----------------------------|
| (a) CLK                     | (b) $\overline{\text{DTR}}$ |
| (c) $\overline{\text{CTS}}$ | (d) $\overline{\text{CS}}$  |

**Codes :**

- (1) (d) (c) (a) (b)
- (2) (c) (b) (d) (a)
- (3) (a) (d) (b) (c)
- (4) (b) (a) (c) (d)

56. Arrange the following in 'C' in the order they can appear logically in a graphics related program :

- (a) restorecrtmode( )
- (b) initgraph( )
- (c) DETECT
- (d) closegraph( )

The correct order of sequence is :

**Codes :**

- (1) (a) (d) (b) (c)
- (2) (c) (b) (d) (a)
- (3) (b) (a) (c) (d)
- (4) (d) (c) (a) (b)

57. Following are microwave bands :

- (a) Ka
- (b) L
- (c) C
- (d) X

Arrange them in descending order of frequencies :

**Codes :**

- (1) (a) (b) (c) (d)
- (2) (b) (d) (c) (a)
- (3) (a) (d) (c) (b)
- (4) (a) (c) (d) (b)

58. Arrange in order of the increasing Bandwidth value for the below mentioned systems :

- |            |         |
|------------|---------|
| (a) DSB-SC | (b) VSB |
| (c) FM     | (d) SSB |

Codes :

- (1) (d) (a) (b) (c)  
 (2) (b) (d) (a) (c)  
 (3) (c) (a) (b) (d)  
 (4) (d) (b) (a) (c)


59. Arrange the below mentioned III-V materials to produce LEDs in order of their increasing emission wavelengths :

- |           |           |
|-----------|-----------|
| (a) In AS | (b) Si C  |
| (c) Ga P  | (d) Ga AS |

Codes :

- (1) (c) (d) (b) (a)  
 (2) (b) (c) (d) (a)  
 (3) (a) (b) (c) (d)  
 (4) (b) (a) (c) (d)

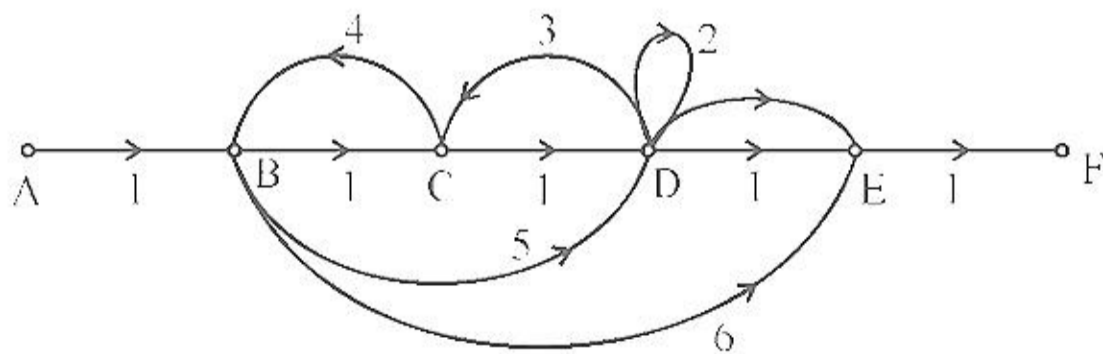60. Consider the following signal flow graph given in the figure :



Let

- A. is no. of forward paths  
 B. is no. of total loops  
 C. is no. of non-touching loop

Arrange above in increasing orders of their values :

- |             |             |
|-------------|-------------|
| (1) A, B, C | (2) B, A, C |
| (3) B, C, A | (4) C, B, A |

**Directions :** Question Nos. 61 – 70 :

The following items consist of two statements, one labelled as “Assertion (A)” and the other labelled as the “Reason (R)”. You are to examine the two statements carefully and decide if the Assertion (A) and the Reason (R) are individually true and if so whether the reason is a correct explanation of the assertion. Select your answer to these items using the codes given below and mark your answer accordingly.

**Codes :**

- (1) Both (A) and (R) are true and (R) is the correct explanation of (A).
- (2) Both (A) and (R) are true, but (R) is not the correct explanation of (A).
- (3) (A) is true, but (R) is false.
- (4) (A) is false, but (R) is true.

**61. Assertion (A) :** In a bipolar IC fabrication, the diode isolation is used to isolate one device from the other.

**Reason (R) :** P<sup>+</sup>n diode used as isolation diode in IC fabrication.

**62. Assertion (A) :** It is convenient to write loop equations for a network containing voltage source but no current source.

**Reason (R) :** If the current sources are present, then these must be first converted into their equivalent voltage sources.

**63. Assertion (A) :** The Gunn diode characteristics shows the region of negative resistance.

**Reason (R) :** The Gunn diode is made of n-type and p-type degenerate semiconductor.

**64. Assertion (A) :** Asynchronous sequential circuit is also called event driven circuit.

**Reason (R) :** Event driven circuit does not have clock to trigger change of state. The states are changed by the change in input signal of the previous stage.

**65. Assertion (A) :** A low  $\overline{WR}$  means a write operation and a low  $\overline{RD}$  means a read operation.

**Reason (R) :**  $\overline{WR}$  and  $\overline{RD}$  both cannot be low at the same time.

66. **Assertion (A) :** In 'C', structures cannot be compared using relational operators == and !=.

**Reason (R) :** A field by field comparison might require unacceptable amounts of repetitive code for large structures. Pointer fields may also cause problems.

67. **Assertion (A) :** Curl of any vector is a vector. It gives normal vector which is perpendicular to both the plane and the parent vector.

**Reason (R) :** The value of  $\text{curl } \vec{H}$  can be found by the following expression :

$$(\text{Curl } \vec{H})_{\text{Normal}} = \lim_{\Delta S \rightarrow 0} \frac{\oint \vec{H} \times d\vec{l}}{\Delta S}$$

Where,  $\Delta S$  is the planar area,  $d\vec{l}$  is line element.

68. **Assertion (A) :** The kind of radio receiver best suited to have the sensitivity and selectivity to fully reproduce the modulating signal at its output is known as superheterodyne receivers.

**Reason (R) :** The transmitted signal at the receiver end becomes very weak due to noise and further it had to share the free space with thousands of other signal and may have to travel a distance.

69. **Assertion (A) :** Those semiconductor materials that practically no thermally generated current carriers at room temperature are used as photoconductors.

**Reason (R) :** These materials are essentially insulators in the dark and carriers generated by the absorption of light cause maximum possible change in the resistivity of the cell.

70. **Assertion (A) :** According to Routh-Hurwitz criterion, the system represented by characteristic equation  $F(S)$  will be unstable, if the first column of the array contains no sign change.

**Reason (R) :** If any row of the Routh's table is multiplied or divided by a positive integer, then the system stability will not be affected.

Now-a-days, electronic measuring instruments are required for all the applications like industrial, medical, biomedical, Aerospace, etc. They are based upon basic principles of measuring resistance, temperature, pH, viscosity, pressure, humidity, etc. They are based on transducers, which convert physical quantity into electrical quantity, which are later on measured and calibrated.

71. The pH value of a solution having a hydrogen ion concentration of  $2.3 \times 10^{-11}$  g/litre is :
- (1) Strong acidic in nature                      (2) Alkaline in nature  
(3) Neutral                                              (4) Slightly acidic
72. The reference electrode in pH measurement is
- (1) Glass electrode                                  (2) Hydrogen electrode  
(3) Antimony electrode                              (4) Hg-Calomel electrode
73. ECG represents :
- (1) the rhythmic curve of depolarisation and repolarisation of the myocardium, the heart muscle.  
(2) the wave form of the voltage produced in the heart muscle due to an externally applied electrical stimulus.  
(3) the record of electrical currents flowing in the cardiac muscle.  
(4) the record of intensity of heart sounds at different intervals sensed by an electro-acoustic sensor.
74. Optical pyrometers are used to measure :
- (1) High intensity                                      (2) Low temperatures  
(3) High temperatures                                (4) Light intensity & high temperatures
75. Which of the following is a positive displacement device ?
- (1) Rotameter                                          (2) Sliding vane flow meter  
(3) Turbine flow meter                                (4) Volumetric tank

Space For Rough Work

**prepp**  
Your Personal Exam Guide