

4.8 (A) $\vec{V} \times \vec{H} = \vec{J}$

(B) $\int_r \vec{E} \cdot \vec{a}_r = -\frac{d}{f} \int_s \vec{B} \cdot \vec{d}s$

(C) $\vec{V} \vec{J} = -\frac{\partial p}{\partial t}$

- (1) Continuity equation
- (2) Faraday's law
- (3) Ampere's Law
- (4) Gauss's law
- (5) Biot-Savart law

ANSWERS

1. 1 (c) 1. 2 (d) 1. 3 (d) 1. 4 (b) 1. 5 (c) 1. 6 (d) 1. 7 (c) 1. 8 (b) 1. 9 (c) 1. 10 (a)
 1. 11 (b) 1. 12 (d) 1. 13 (c) 1. 14 (d) 1. 15 (a) 1. 16 (c) 1. 17 (b) 1. 18 (c) 1. 19 (a)

EXPLANATIONS


1.3 Voltage across the capacitor

$$= \frac{200}{\sqrt{R^2 + (X_L - X_C)^2}} \times (-jX_C)$$

$$= \frac{200}{\sqrt{100 + (20 - 20)^2}} \times (-j20)$$


$$= -j400$$

$$= 400 \angle -90^\circ \text{ V}$$

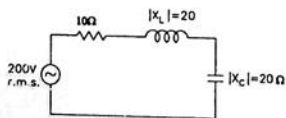

$$= \frac{2}{s(2 \times 10^{-2}s + 1)} \approx \frac{2}{s}$$

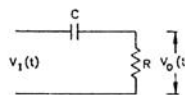$V_o(t) = 2u(t)$
 \therefore Maximum voltage = 2 V



1.4 In the Laplace domain,

$$V_o(s) = \frac{V_i(s)}{R + \frac{1}{Cs}} \times R$$

$$= \frac{V_i(s) RCs}{RCs + 1}$$

$$V_i(t) = 100t u(t)$$

and $V_i(s) = \frac{100}{s^2}$

Hence, $V_o(s) = \frac{100}{s^2} \left[\frac{5 \times 10^3 \times 10^{-6} s}{5 \times 10^3 \times 4 \times 10^{-6} s + 1} \right]$

1.5 $H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$

$$H(j\omega) = \frac{\omega_n^2}{-\omega^2 + 2\zeta\omega_n j\omega + \omega_n^2}$$

$$|H(j\omega)| = \frac{\omega_n^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + (2\zeta\omega_n\omega)^2}}$$

$|H(j0)| = 1$

If ω_c is the 3 - dB frequency, then

$$|H(j\omega_c)| = \frac{\omega_n^2}{\sqrt{(\omega_n^2 - \omega_c^2)^2 + (2\zeta\omega_n\omega_c)^2}} = 0.707$$