

Electrostatics JEE Main PYQ – 1

Total Time: 25 Minute

Total Marks: 40

Instructions

Instructions

1. Test will auto submit when the Time is up.
2. The Test comprises of multiple choice questions (MCQ) with one or more correct answers.
3. The clock in the top right corner will display the remaining time available for you to complete the examination.

Navigating & Answering a Question

1. The answer will be saved automatically upon clicking on an option amongst the given choices of answer.
2. To deselect your chosen answer, click on the clear response button.
3. The marking scheme will be displayed for each question on the top right corner of the test window.

Electrostatics

1. Two equal capacitors are first connected in series and then in parallel. The ratio of the equivalent capacities in the two cases will be: (+4, -1)

[24 Feb 2021 shift1]

- a. 4:01
- b. 2:01
- c. 1:04
- d. 1:02

2. A charge Q is distributed over two concentric conducting thin spherical shells radii r and R ($R > r$). If the surface charge densities on the two shells are equal, the electric potential at the common centre is : (+4, -1)

[Sep. 02, 2020 (II)]

- a. $\frac{1}{4\pi\epsilon_0} \frac{(R+2r)Q}{2(R^2+r^2)}$
- b. $\frac{1}{4\pi\epsilon_0} \frac{(R+r)}{2(R^2+r^2)} Q$
- c. $\frac{1}{4\pi\epsilon_0} \frac{(R+r)}{(R^2+r^2)} Q$
- d. $\frac{1}{4\pi\epsilon_0} \frac{(2R+r)}{(R^2+r^2)} Q$

3. A parallel plate capacitor is of area 6 cm^2 and a separation 3 mm . The gap is filled with three dielectric materials of equal thickness (see figure) with dielectric constants $K_1 = 10$, $K_2 = 12$ and $K_3 = 14$. The dielectric constant of a material which when fully inserted in above capacitor, gives same capacitance would be : (+4, -1)

[10 Jan. 2019 I]

- a. 12
- b. 4
- c. 36
- d. 14


4. A parallel plate capacitor with square plates is filled with four dielectrics of dielectric constants K_1, K_2, K_3, K_4 arranged as shown in the figure. The effective dielectric constant K will be : (+4, -1)

[9 Jan 2019 II]

- a. $K = \frac{(K_1+K_2)(K_3+K_4)}{2(K_1+K_2+K_3+K_4)}$
- b. $K = \frac{(K_1+K_2)(K_3+K_4)}{(K_1+K_2+K_3+K_4)}$
- c. $K = \frac{(K_1+K_4)(K_2+K_3)}{2(K_1+K_2+K_3+K_4)}$
- d. $K = \frac{(K_1+K_3)(K_2+K_4)}{K_1+K_2+K_3+K_4}$

5. Figure shows a network of capacitors where the numbers indicates capacitances in micro Farad. The value of capacitance C if the equivalent capacitance between point A and B is to be $1 \mu F$ is : (+4, -1)





[Online April 10, 2016]

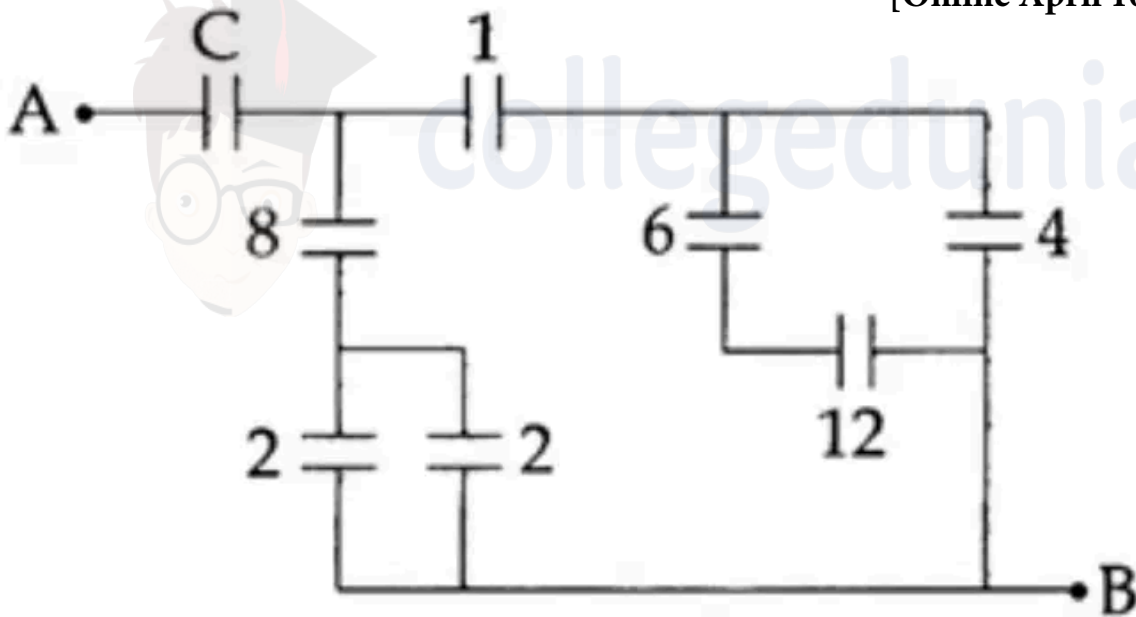

- a. $\frac{31}{23} \mu F$
- b. $\frac{32}{23} \mu F$
- c. $\frac{33}{23} \mu F$
- d. $\frac{34}{23} \mu F$

6. In the given circuit, charge Q_2 on the $2\mu F$ capacitor changes as C is varied from $1\mu F$ to $3\mu F$. Q_2 as a function of ' C ' is given properly by (figures are drawn schematically and are not to scale) (+4, -1)

[2015]

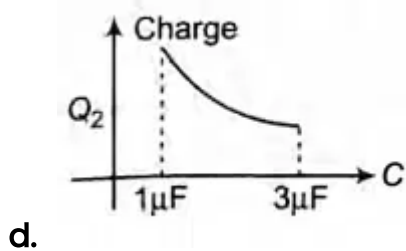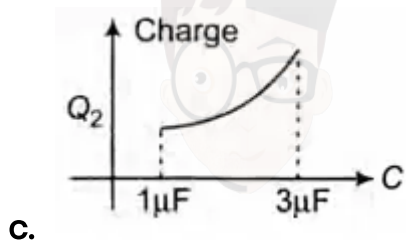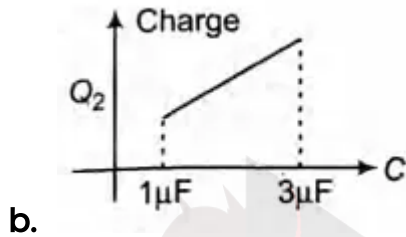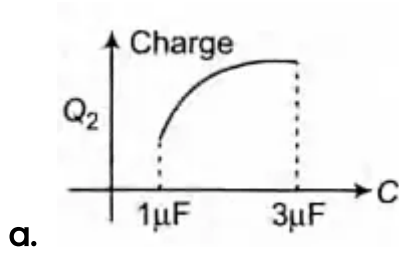

7. A combination of capacitors is set up as shown in the figure. The magnitude of the electric field, due to a point charge Q (having a charge equal to the sum of the charges on the $4\mu F$ and $9\mu F$ capacitors), at a point distant 30 m from it, would equal : (+4, -1)

[2016]

- a. 240 N/C

- b. 360 N/C
- c. 420 N/C
- d. 480 N/C

8. A capacitance of $2 \mu F$ is required in an electrical circuit across a potential difference of $1.0 kV$. A large number of $1 \mu F$ capacitors are available which can withstand a potential difference of not more than $300 V$. The minimum number of capacitors required to achieve this is : (+4, -1)

[2017]

- a. 2
- b. 16
- c. 24
- d. 32

9. A capacitor of capacitance $900 \mu F$ is charged by a $100 V$ battery. The capacitor is disconnected from the battery and connected to another uncharged identical capacitor such that one plate of uncharged capacitor connected to positive plate and another plate of uncharged capacitor connected to negative plate of the charged capacitor. The loss of energy in this process is measured as $x \times 10^{-2} J$. The value of x is _____ (+4, -1)

[30-Jan-2023 Shift 1]

10. A capacitor has capacitance $5 \mu F$ when its parallel plates are separated by air medium of thickness d . A slab of material of dielectric constant 15 having area equal to that of plates but thickness $\frac{d}{2}$ is inserted between the plates. Capacitance of the capacitor in the presence of slab will be _____ μF (+4, -1)

[25-Jan-2023 Shift 2]

Answers

1. Answer: c

Explanation:

For series combination

$$\frac{1}{C_{eq1}} = \frac{1}{C} + \frac{1}{C}$$

$$\Rightarrow C_{eq1} = \frac{C}{2}$$

For parallel combination

$$C_{eq2} = C + C$$


$$\Rightarrow C_{eq2} = 2C$$

$$\Rightarrow \frac{C_{eq1}}{C_{eq2}} = \frac{C/2}{2C} = \frac{1}{4} = 1 : 4$$

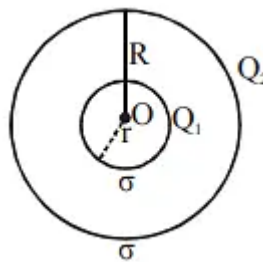2. Answer: c

Explanation:

Let the charges on inner and outer spheres are Q_1 and Q_2



Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.
- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing ability of capacitors, and the unit in which they are measured is "farads".

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series

Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor's capacitance.

In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor's capacitance.

3. Answer: a

Explanation:

Let dielectric constant of material used be K .

$$\therefore \frac{10\epsilon_0 A/3}{d} + \frac{12\epsilon_0 A/3}{d} + \frac{14\epsilon_0 A/3}{d} = \frac{K\epsilon_0 A}{d}$$
$$\Rightarrow K = 12$$

Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.
- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing ability of capacitors, and the unit in which they are measured is "farads".

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series

Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor's capacitance.

In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor's capacitance.

4. Answer: d

Explanation:

$$C_{12} = \frac{C_1 C_2}{C_1 + C_2} = \frac{\frac{k_1 \in_0 \frac{L}{2} \times L}{d/2} \cdot \frac{k_2 \left[\in_0 \frac{L}{2} \times L \right]}{d/2}}{(k_1 + k_2) \left[\frac{\in_0 \cdot \frac{L}{2} \times L}{d/2} \right]}$$

$$C_{12} = \frac{k_1 k_2 \in_0 L^2}{k_1 + k_2 d}$$

in the same way we get, $C_{34} = \frac{k_3 k_4 \in_0 L^2}{k_3 + k_4 d}$

$$\therefore C_{eq} = C_{12} + C_{34} = \left[\frac{k_1 k_2}{k_1 + k_2} + \frac{k_3 k_4}{k_3 + k_4} \right] \frac{\in_0 L^2}{d}$$

....(i)

Now if $k_{eq} = k$, $C_{eq} = \frac{k \in_0 L^2}{d}$ (ii)

on comparing equation (i) to equation (ii), we get

$$k_{eq} = \frac{k_1 k_2 (k_3 + k_4) + k_3 k_4 (k_1 + k_2)}{(k_1 + k_2)(k_3 + k_4)}$$

This does not match with any of the options so probably they have assumed the wrong combination

$$C_{13} = \frac{k_1 \in_0 L \frac{L}{2}}{d/2} + k_3 \in_0 \frac{L \cdot \frac{L}{2}}{d/2}$$

$$= (k_1 + k_3) \frac{\in_0 L^2}{d}$$

$$C_{24} = (k_2 + k_4) \frac{\in_0 L^2}{d}$$

$$C_{eq} = \frac{C_{13} C_{24}}{C_{13} + C_{24}} = \frac{(k_1 + k_3)(k_2 + k_4) \in_0 L^2}{(k_1 + k_2 + k_3 + k_4) d}$$

$$= \frac{k \in_0 L^2}{d}$$

$$k = \frac{(k_1 + k_3)(k_2 + k_4)}{(k_1 + k_2 + k_3 + k_4)}$$

However this is one of the four options. It must be a "Bonus" logically but of the given options probably they might go with (4)

Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.
- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing

ability of capacitors, and the unit in which they are measured is “farads”.

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series

Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor’s capacitance.

In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor’s capacitance.

5. Answer: b

Explanation:

$$\frac{8 \times 12}{18} = 4 \mu F$$

Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.
- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing ability of capacitors, and the unit in which they are measured is "farads".

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series

Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor's capacitance.

In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor's capacitance.

6. Answer: a

Explanation:

$$q = \left(\frac{3C}{C+3}\right) E$$

$$q = CV$$

$$q \propto C$$

$$q_2 = \left(\frac{3C}{C+3}\right) E \left(\frac{2}{3}\right)$$

$$q_2 = \left(\frac{2C}{C+3}\right) E$$

$$q_2 = \left(\frac{2c}{1+\frac{3}{c}}\right) E \quad q = CV$$

$$C \uparrow q_2 \uparrow$$

If $C \rightarrow \infty, q = \text{constant value.}$

Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.
- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing ability of capacitors, and the unit in which they are measured is "farads".

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series


Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor's capacitance.

In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor's capacitance.

7. **Answer: c**

Explanation:

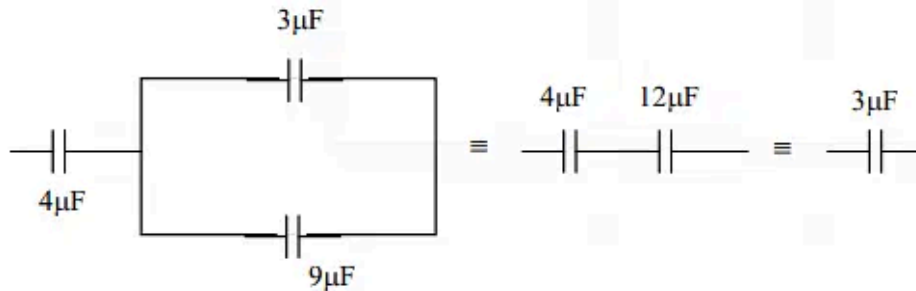

The equivalent capacitance of the above branch will be $\frac{4(9+3)}{4+9+3} = 3\mu\text{F}$

The total charge in the above branch will be $Q = CV = 24\mu\text{F}$

Now voltage across $12\mu\text{F}$ $V = \frac{Q}{C} = \frac{24}{12} = 2\text{V}$

This is the same as the voltage across $9\mu\text{F}$ capacitor.

Hence, the charge on $9\mu\text{F}$ capacitor is $= 24 + 18 = 42\mu\text{C}$

Now by Coulomb's law,

$$E = \frac{kQ}{r^2}$$

$$E = \frac{9 \times 10^9 \times 42 \times 10^{-6}}{30^2} = 420 \text{ N/C}$$

Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.
- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing ability of capacitors, and the unit in which they are measured is "farads".

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series

Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor's capacitance.

In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor's capacitance.

8. Answer: d

Explanation:

Following arrangement will do the needful :

8 capacitors of $1 \mu F$ in parallel with four such branches in series.

Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.

- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing ability of capacitors, and the unit in which they are measured is "farads".

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series

Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor's capacitance.


In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor's capacitance.

9. Answer: 225 – 225

Explanation:

The correct answer is 225.


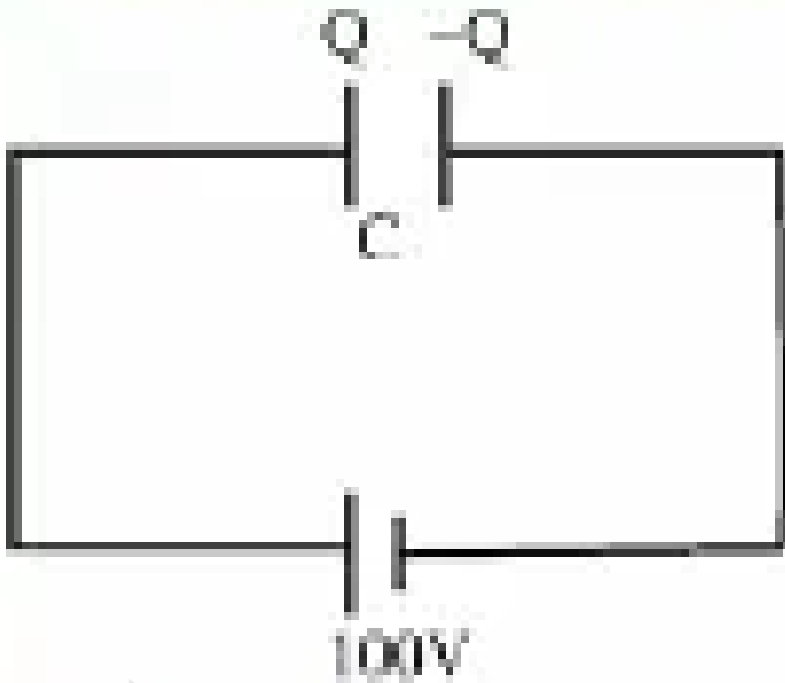



$C = 900 \mu\text{F}$

$Q = CV = 900 \times 10^{-6} \times 100 = 9 \times 10^{-2} = 90 \text{ mC}$

Now

$90 \text{ mC} \quad -90 \text{ mC}$

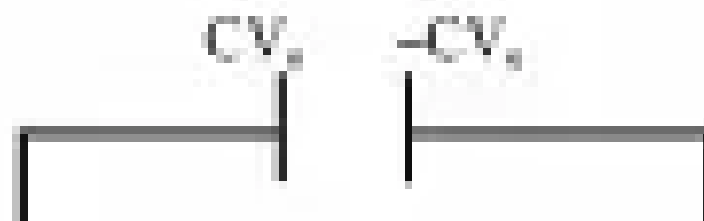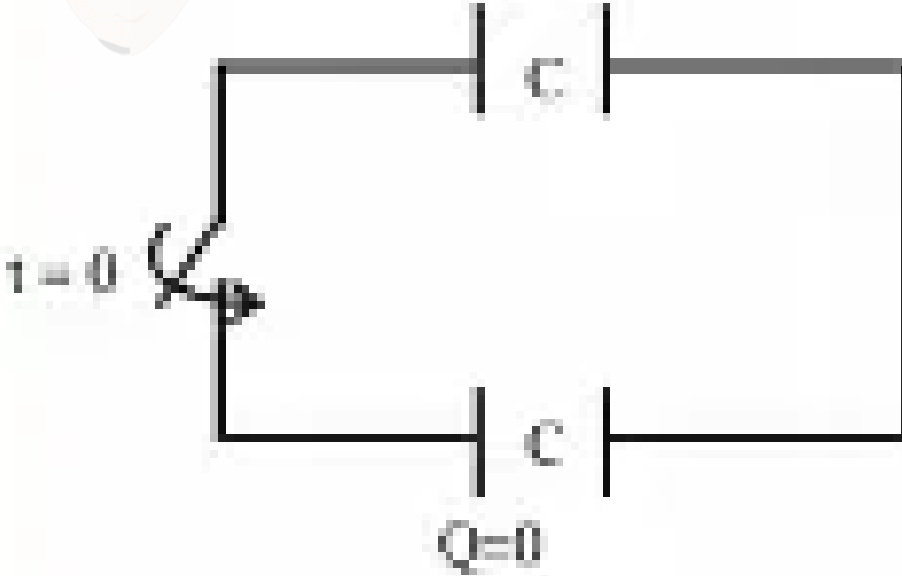

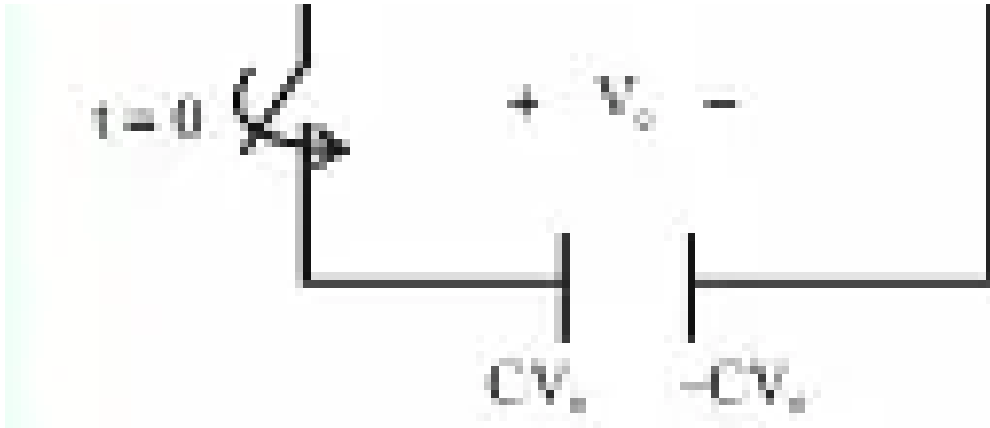


Common potential will be developed across both capacitors by kVL

Total charge on left plates of capacitors should be conserved.

$$\therefore 90 mc + 0 = 2cv_0$$

$$cv_0 = 45 mc$$

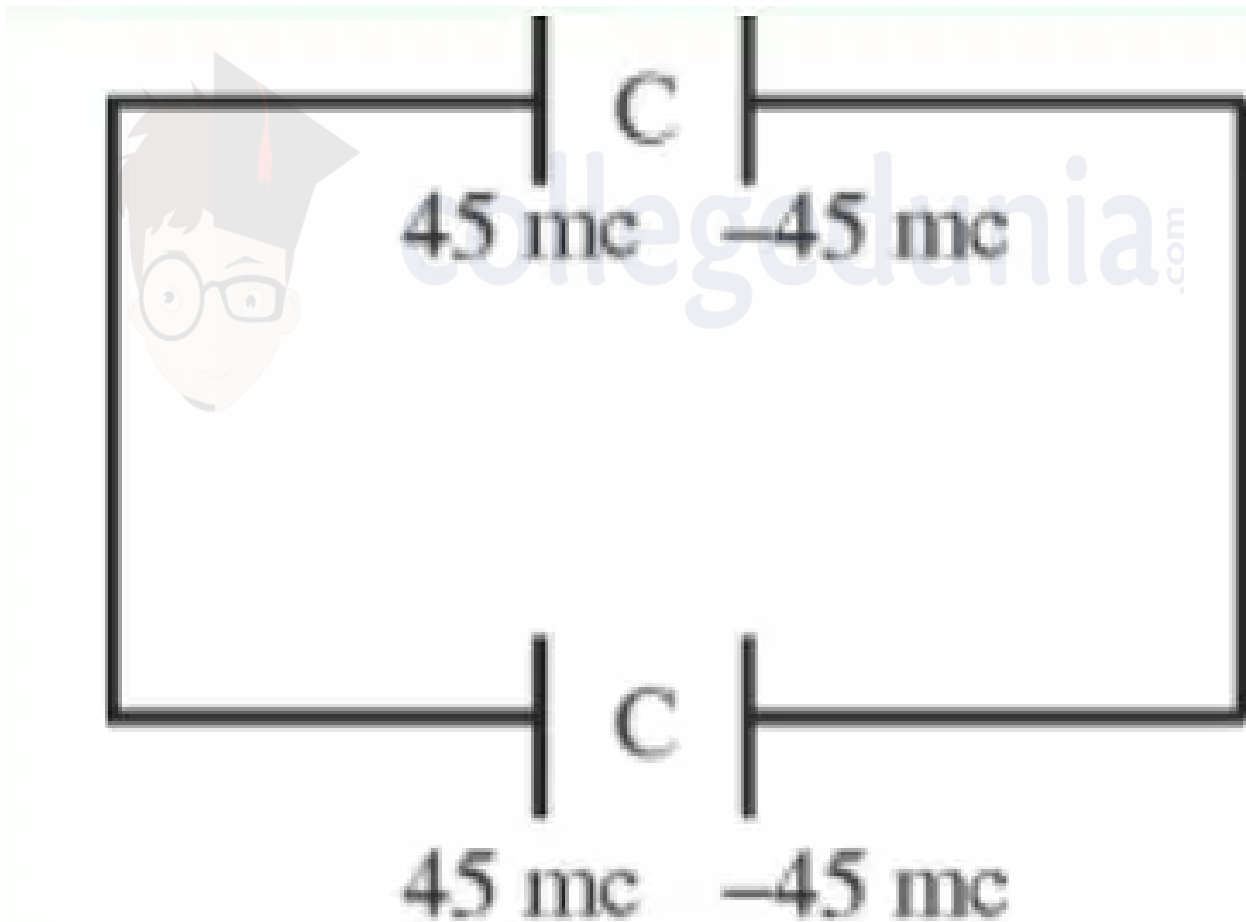

Heat dissipated = $U_i - U_f$ [Change in energy stored in the capacitors]

$$= \frac{1}{2} \frac{(90mc)^2}{900\mu F} - 2 \times \frac{1}{2} \frac{(45mc)^2}{900\mu F} \left[U = \frac{Q^2}{2c} \right]$$

$$= \frac{1}{2 \times 900 \times 10^{-6}} (8100 - 4050) \times 10^{-6}$$

$$= 2.25 \text{ Joule}$$

OR

$$\begin{aligned}\text{Heat} &= \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2 \\ &= \frac{1}{2} \frac{C^2}{2C} (100 - 0)^2 \\ &= \frac{1}{2} \frac{900 \times 10^{-6}}{2} \times 10^4 = \frac{9}{4} \text{ Joule} = 2.25 \text{ Joule}\end{aligned}$$

Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.
- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing ability of capacitors, and the unit in which they are measured is "farads".

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series

Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor's capacitance.



In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor's capacitance.

10. Answer: 6 – 6

Explanation:

The correct answer is 6.

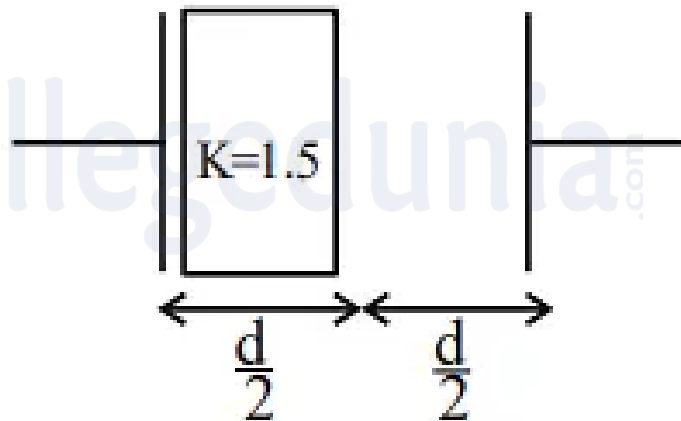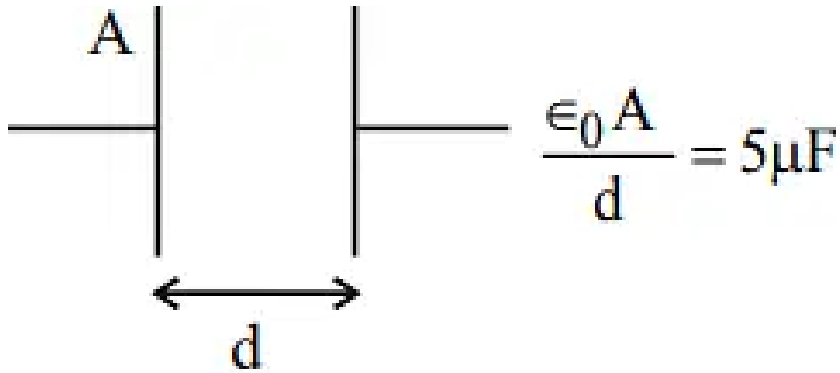

$$C_{\text{new}} = \frac{\epsilon_0 A}{\left(\frac{d}{2}\right) + \left(\frac{d}{2}\right)}$$

$$= \frac{\epsilon_0 A}{1.5 \times \frac{d}{2} + \frac{d}{2}}$$

$$= \frac{\epsilon_0 A}{\left(\frac{d}{3} + \frac{d}{2}\right)} = \frac{6\epsilon_0 A}{5d}$$

$$= \frac{6}{5} \times 5\mu F = 6\mu F$$

Concepts:

1. Electrostatic Potential and Capacitance:

Electrostatic Potential

The potential of a point is defined as the **work done** per unit charge that results in bringing a charge from infinity to a certain point.

Some major things that we should know about electric potential:

- They are denoted by V and are a scalar quantity.
- It is measured in volts.

Capacitance

The ability of a **capacitor** of holding the energy in form of an **electric charge** is defined as capacitance. Similarly, we can also say that capacitance is the storing ability of capacitors, and the unit in which they are measured is "farads".

Read More: [Electrostatic Potential and Capacitance](#)

The capacitor is in Series and in Parallel as defined below;

In Series

Both the Capacitors C_1 and C_2 can easily get connected in series. When the **capacitors are connected in series** then the total capacitance that is C_{total} is less than any one of the capacitor's capacitance.

In Parallel

Both Capacitor C_1 and C_2 are connected in parallel. When the capacitors are connected parallelly then the total capacitance that is C_{total} is any one of the capacitor's capacitance.