### POST GRADUATE COMMON ENTRANCE TEST - 2011

DATE and TIME		COURSE	SUBJECT
06-08-2011 10:30 am to 12:30 pm		ME / M. Tech / rastructure Management ered by VTU / UVCE / UBDT	
MAXIMUM MARKS	askati rent	TOTAL DURATION	MAXIMUM TIME FOR ANSWERING
100		150 Minutes	120 Minutes
MENTION YOUR PGC	ET NO.	QUESTION	BOOKLET DETAILS
3 10H 33W   1		VERSION CODE	SERIAL NUMBER
eT mort		<b>A</b> <sub>3</sub>	00006435

#### DOs

- Check whether the PGCET No. has been entered and shaded in the respective circles on the OMR answer sheet.
- 2. This question booklet is issued to you by the invigilator after the 2nd Bell, i.e. after 10:25 am.
- 3. The serial number of this question booklet should be entered on the OMR answer sheet.
- 4. The version code of this question booklet should be entered on the OMR answer sheet and the respective circles should also be shaded completely.
- Compulsorily sign at the bottom portion of the OMR answer sheet in the space provided.

#### DON'Ts

- The timing and marks printed on the OMR answer sheet should not be damaged / mutilated / spoiled.
- The 3rd Bell rings at 10:30 am, till then;
  - Do not remove the seals of this question booklet.
  - Do not look inside this question booklet.
  - Do not start marking on the OMR answer sheet.

#### IMPORTANT INSTRUCTIONS TO CANDIDATES

- This question booklet contains 75 (items) questions and each question will have one statement and four answers. (Four different options / responses.)
- 2. After the 3rd bell is rung at 10:30 am, remove the seals of this question booklet and check that this booklet does not have any unprinted or torn or missing pages or items etc., if so, get it replaced by a complete test booklet. Read each item and start marking on the OMR answer sheet.
- During the subsequent 120 minutes
  - Read each question (item) carefully.
  - Choose one correct answer from out of the four available responses (options / choices) given under each question / item. In case you feel that there is more than one correct response, mark the response which you consider the best. In any case, choose only one response for each question / item.
  - Completely darken / shade the relevant circle with a blue or black ink ballpoint pen against the question number on the OMR answer sheet.
- 4. Please note that even a minute unintended ink dot on the OMR answer sheet will also be recognized and recorded by the scanner. Therefore, avoid multiple markings of any kind on the OMR answer sheet.
- Use the space provided at the bottom on each page of the question booklet for Rough Work. Do not use the OMR answer sheet for the same.
- After the last bell is rung at 12:30 pm, stop marking on the OMR answer sheet and affix your left hand thumb impression on the OMR answer sheet as per the instructions.
- Hand over the OMR answer sheet to the room invigilator as it is.
- 8. After separating the top sheet (KEA copy), the invigilator will return the bottom sheet replica (candidate's copy) to you to carry home for self evaluation.
- 9. Preserve the replica of the OMR answer sheet for a minimum period of ONE year.
- 10. Only Non-programmable calculators are allowed.
- 11. Please note this Question Booklet consists of sub-branches. Total number of questions is 75. Question Nos. 1 to 45 is compulsory and common to all the branches. Candidate has to answer any one paper from Question Nos. 46 - 75 out of the sub-branches as opted, by him/her in the Application Form.

#### Marks Distribution

PART – A: (Section-I) 30 Questions:  $30 \times 1 = 30$ ; (Section-II): 15 Questions:  $15 \times 2 = 30$ PART - B: (Section-I) 20 Questions:  $20 \times 1 = 20$ ; (Section-II): 10 Questions:  $10 \times 2 = 20$ 

P.T.O.





Electrical Sciences

# ELECTRICAL SCIENCES

#### IMPORTANT INSTRUCTIONS AND BRANCHWISE INDEX FOR THE CANDIDATES

Question Nos. 1 to 45 is compulsory and common to all the branches. Question Nos. 46 to 75 are optional. Sub-branches are there in this Booklet. The candidate has to opt any one branch according to his/her Application Form.

RIBER	GSA30000 Subject		Page	Page No.	
Sub- branch			From	То	
1.	Electrical and El	17	22		
2.	Electronics and	% C) 23	28		
Balkon	Telecommunicat	use sense bes open			
3.	Bio-Medical Eng	29	34		
	Medical Electron	ics (ME)			
4.	Instrumentation	Technology (IT)	35	39	

of page 4 stables of earliest tests maked out muter live estables out your Audit

rease note this One stem Soundet consists of sub-fire consist data number of entestions is 75. Onesementary to



#### PART - A

# ( Common to E&E/E&C/TC/BME/ME/IT ) SECTION - I

Each question carries one mark.

 $30 \times 1 = 30$ 

1.  $\int (2\cos x - 4\sin x) \, dx \text{ is}$ 


(A)  $2\sin x + 4\cos x$ 

(B)  $2\sin x - 4\cos x$ 

(C)  $2\sin x - 4\cos x + c$ 

(D)  $2\sin x + 4\cos x + c$ .

2.

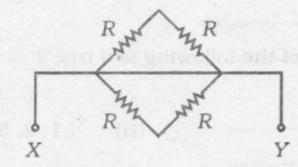

The resistance between x-y terminals is


(A) R

(B)  $\frac{F}{2}$ 

(C) zero

(D)  $\frac{R}{4}$ .

3.

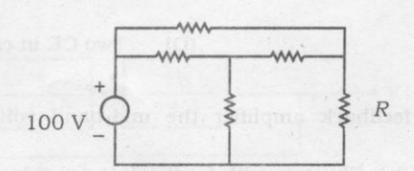

In the figure, the power dissipated by the resistor R is 10 W. If the voltage is increased to 110 V, the power dissipated will be

(A) 12·1 W


(B) 21 W

(C) 20 W

(D) depends on value of R.

- 4. In a series RLC circuit, we get a leading power factor current
  - (A) at resonant frequency
- (B) at less than resonant frequency
- (C) at greater than resonant frequency (D)
- at all frequencies.

5.

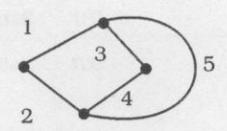

In the graph shown which of the following is a tree?

(A) {1,2,3}

(B) {1,2,5}

(C) {3, 4, 5}

- (D) {1, 2, 3, 4}.
- 6. In a transistor configuration, the voltage gain is found to be 1. The configuration is
  - (A) CE

(B) CB

(C) CC


- (D) Two CE in cascade.
- 7. In a voltage-series feedback amplifier the mid-band voltage gain is 1200. The feedback factor  $\beta$  = 0·1. The gain with feedback is equal to
  - (A) 1200

(B) -120


(C) -991·7


(D) -9.917.

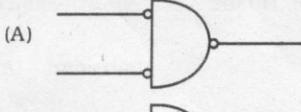- 8. The distortion introduced by the non-linear dynamic transfer characteristics may be reduced using
  - (A) push-pull amplifier configuration
  - (B) positive feedback amplifier
  - (C) cascading amplifier
  - (D) increasing source impedance.
- 9. Which of the following represents a NAND gate?



(B)

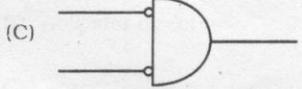

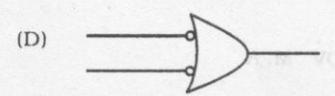


- 10. The BCD code for decimal number 12 is
  - (A) 00001100

(B) 10000010

(C) 00010010

(D) 11000000.

11.

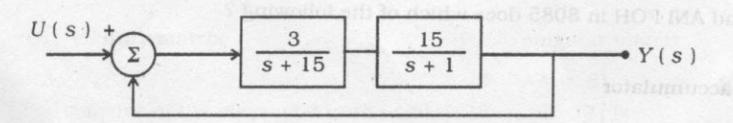

The steady state error in the response of the above system to a unit step input is

(A) 25%

(B) 0.75%

(C) 6%

(D) 33%.

12. A code segment of 8085 is given below:

LXI H, 3FFE

MOV B, M

INR L

MOV A, M

ADD B

INR L

MOV M, A

On completion of execution, the result of addition is found in

(A) register A

(B) location 2FFE

(C) location 2F00

- (D) location 3000.
- 13. The command ANI FOH in 8085 does which of the following?
  - (A) Clears accumulator
  - (B) Clears the lower nibble of the accumulator
  - (C) Clears the upper nibble of the accumulator
  - (D) Sets the lower nibble of the accumulator.

IIV (A)

- 14. The contents of the accumulator in 8085 is A7 and CY = 0. After the execution of the instruction RLC, the contents of accumulator and CY are
  - (A) [A] = A8; CY = 0
  - (B) [A] = 4E; CY = 1
  - (C) [A] = 4F; CY = 0
  - (D) [A] = A8; CY = 1.
- The instruction STA 2080H, in 8085 is of which addressing mode?
  - (A) Immediate
  - (B) Register direct
  - (C) Direct
  - (D) Register indirect.
- 21. A voltage source is connected across an ideal inductor. The current through the The matrix 2 is a/an tuductor is observed to be a constant. The voltage source mus 0be
  - (A) symmetric matrix
- skew-symmetric matrix (B)

7 is

(C) identity matrix

- singular matrix. (D)
- 3(s+10), in the frequency domain. The value The current in a circuit 6 to 4-by 17. The cofactor of the element 8 in the matrix 2 5 8

A 0

(A) - 9

(B)

(C) 33

A 8 (D) -33.

- 18. The angle  $\theta$  between two vectors  $\vec{a}$  and  $\vec{b}$  is given by
  - (A)  $\cos \theta = \frac{|\vec{a} \times \vec{b}|}{|\vec{a} \cdot \vec{b}|}$

(B)  $\cos \theta = \frac{|\vec{a} \times \vec{b}|}{|\vec{a}||\vec{b}|}$ 

(C)  $\tan \theta = \frac{|\vec{a} \times \vec{b}|}{|\vec{a}||\vec{b}|}$ 

- (D)  $\sin \theta = \frac{|\vec{a} \times \vec{b}|}{|\vec{a}||\vec{b}|}$
- 19. The magnitude of the position vector of the point (2, 3, -4) is
  - (A) √11

(B) (

(C) √29

- (D) 1
- 20. The solution of the equation  $x + y \frac{dy}{dx} = 0$  is
  - $(A) \quad x + y = k$

 $(B) \qquad x^2 + y^2 = k$ 

(C)  $\sqrt{x} + \sqrt{y} = k$ 

- (D) ln(x+y)=k.
- 21. A voltage source is connected across an ideal inductor. The current through th inductor is observed to be a constant. The voltage source must be
  - (A) sinusoidal

(B) ramp

(C) step

- (D) impulse.
- 22. The current in a circuit is given by  $I(s) = \frac{3(s+10)}{s(s+12)}$ , in the frequency domain. The value

of l(t) as  $t \to \infty$  is

(A) 0.5 A

(B) 0 A

(C) 3 A

(D) 2.5 A.

- 23. The relationship between the electric field intensity and the potential is given by
  - $E = -\nabla V$

(B)  $E = \int V \cdot dl$ 

(C)  $E = \nabla^2 V$ 

- $E = \nabla \times V$ . (D)
- A full-wave rectifier circuit is supplied by a centre-tap transformer. The peak voltage 24. from end terminal to centre tap is 135 V. Neglecting the forward resistance of the diode, the d.c. output voltage is
  - (A) 135 V

(B) 95.45 V


(C) 85.94 V

- 270 V. (D)
- In a fixed bias circuit,  $V_{CC} = 12 \text{ V}$  and  $R_b = 1 \text{ M}\Omega$ . If an n-p-n silicon transistor is used, 25. the base current  $I_B$  is equal to
  - (A) 12 μA

11.4 μΑ (B)

(C) 12 A

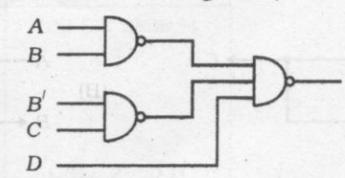- (D) 3.46 µA.
- The output of the network shown below is given by 26.



(A)  $AB + B^{\prime}C + D$ 

(B)  $AB + B^{\prime}C + D^{\prime}$ 


- (C) (A+B)(B'+C)(D) (D) (A+B)(B'+C)(D').
- A counter is designed with T flip-flops. The present state is '011' and the next state is 27. '010'. The input to the T flip-flop to have correct state transition at the next clock pulse is
  - 001 (A)

011 (B)

(C) 010

(D) 111.

28.

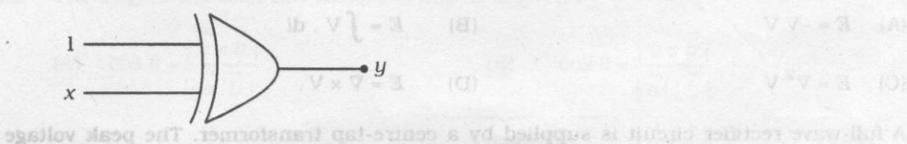

In the above gate the relation between x and y is


(A) y = x

(B) y = 1 and y = 1 and y = 1


(C) y = x


(D) y = 0.


29.

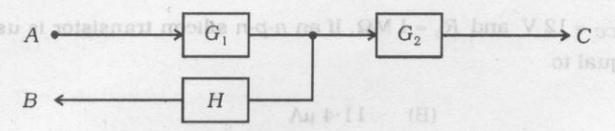

The equivalent for the block diagram is

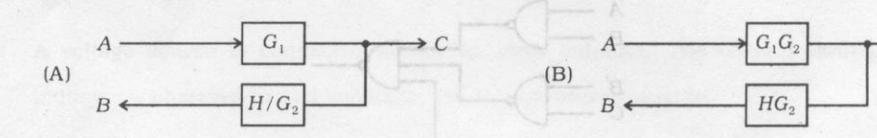

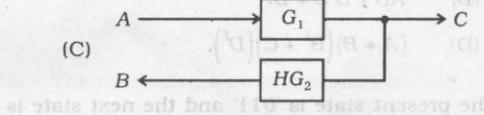

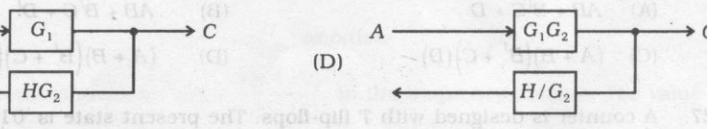

- 30. The characteristic equation of a system is given by  $2s^4 + s^3 + 3s^2 + 5s + 7 = 0$ . The number of roots that lie in the right half of s plane is
  - (A) zero

(B) 2

(C) 4

O.T.9


(D) 1.

#### SECTION - II

Each question carries two marks.

 $15 \times 2 = 30$ 

31.

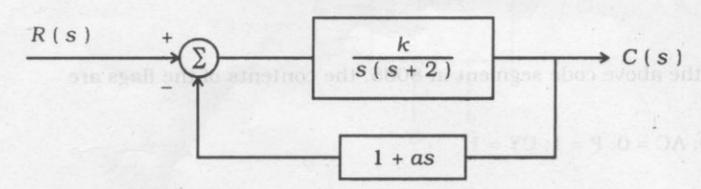

In the above figure damping ratio  $\xi = 0.7$  and undamped natural frequency  $\omega_n = 4 \text{ rad/sec.}$  The values of k and a are

(A) 
$$k = 16, a = 0.225$$

(B) 
$$k = 8, a = 0.225$$

(C) 
$$k = 16$$
,  $a = 0.455$ 

(D) 
$$k = 64, a = 0.9$$

32.

C

Address	Instruction
2000	LXI SP, 2800 H
2040	CALL 2060 H
	99
	100

In the above segment of 8085, what are the contents of the stack and stack pointer after CALL instruction is executed?

(A) 2040, 2800

2041, 2401 (B)

- (C) 2060, 2800 (D) 2043, 27FE.

33. MVI B, 96H

MVI A, 97H

ADD B

On execution of the above code segment in 8085, the contents of the flags are

(A) 
$$S = 0$$
;  $Z = 0$ ;  $AC = 0$ ;  $P = 1$ ;  $CY = 1$ 

(B) 
$$S = 1$$
;  $Z = 1$ ;  $AC = 0$ ;  $P = 0$ ;  $CY = 1$ 

(C) 
$$S = 0$$
;  $Z = 0$ ;  $AC = 0$ ;  $P = 0$ ;  $CY = 1$ 

(D) 
$$S = 0$$
;  $Z = 1$ ;  $AC = 0$ ;  $P = 1$ ;  $CY = 1$ .

34. The characteristic table of an X-Y flip-flop is given below to be implemented using J-K flip-flop. The J-K inputs are

X	Y	$g_{n+1}$
0	0	1
0	1	$Q_n$
1	0	$\overline{Q}_n$
alimano:	ini jas ii	0

(A) J = X;  $K = \overline{Y}$ 


(B)  $J = \overline{X}$ ; K = Y

- (C) J = Y;  $K = \overline{X}$
- (D)  $J = \overline{Y}$ ; K = X.

5000

a\bai 8 0 (A)

35.

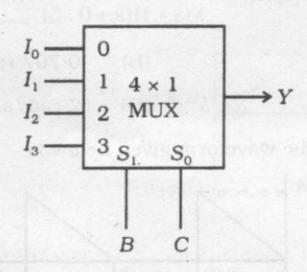


(A) 01AA'

(B) 10 A A'

(C) 00 A' A

(D) 11 A' A. awarb fasture and add

36.

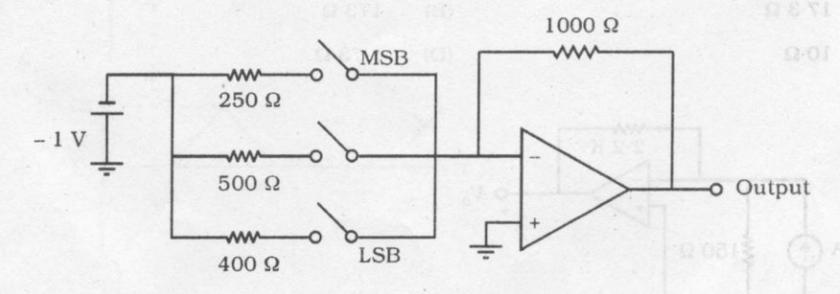

For switch position 1 1 0 (1 is close and 0 is open ) the output voltage is

(A) 2 V

(B) 4 V

(C) 6 V

(D) 0 V.

SPACE FOR ROUGH WORK

collegedunia

37. For the transfer function  $G(s)H(s) = \frac{1}{s(s+1)(s+0.5)}$  the phase cross-over frequency is


(A) 0.5 rad/s

(B) 0.707 rad/s

(C) 1.732 rad/s

(D) 2 rad/s.

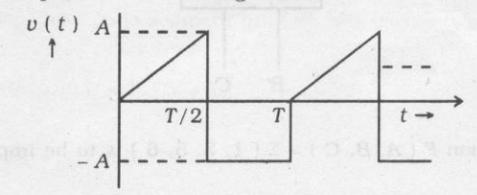38. The rms value of the periodic waveform given below is



(A)  $\sqrt{\frac{2}{3}}A$ 

(B)  $\sqrt{\frac{3}{2}} A$ 

(C)  $\sqrt{\frac{1}{3}} A$ 

(D)  $\sqrt{2} A$ .

39. The line current drawn by a balanced star connected resistive load from a 173 V 3-4 supply is 10 A. The load resistance per phase is


(A) 17·3 Ω

(B) 173 Ω

(C) 10 Ω

(D) 1.73 Ω.

40.

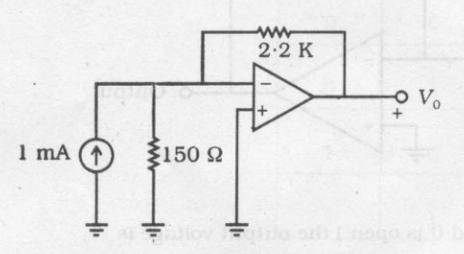


In the circuit  $v_0$  is equal to

(A) 2·2 V


(B) - 2·2 V


(C) 1.5 V


(D) -1.5 V.

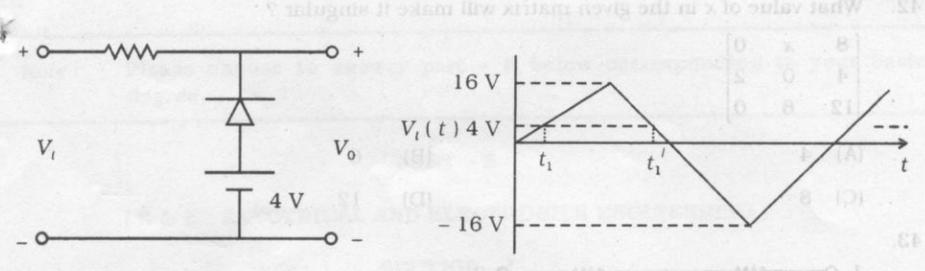


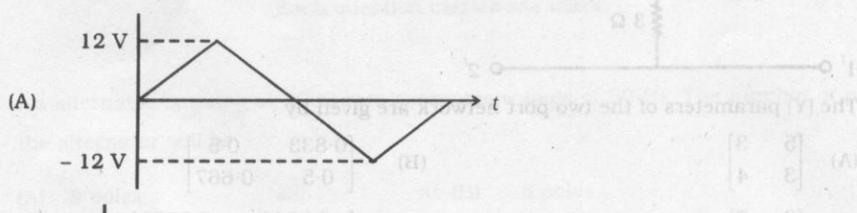In the circuit shown, the output voltage  $v_0$  for the given input is



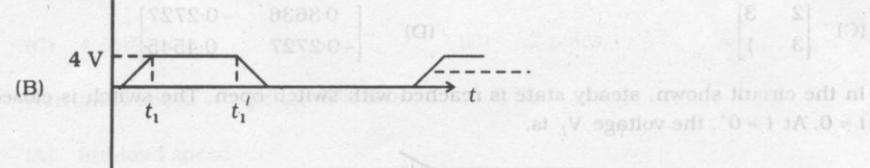

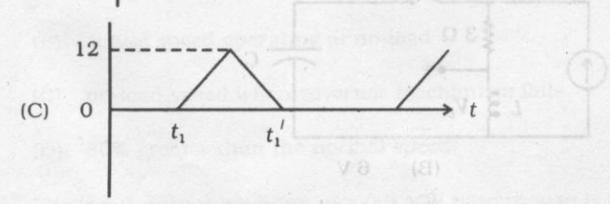

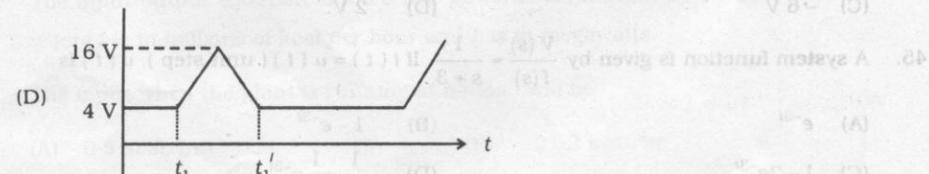

42. What value of x in the given matrix will make it singular?


[8]	x	0]
8	0	2
12	6	0 2 0

- (A) 4
  - A CONTRACTOR
- (C) 8

- (B)
- (D) 12.

6

43.

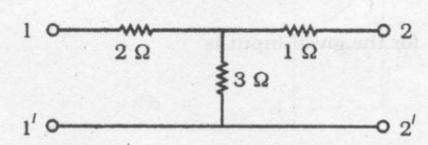


The [Y] parameters of the two port network are given by

- $(A) \quad \begin{bmatrix} 5 & 3 \\ 3 & 4 \end{bmatrix}$
- (C)  $\begin{bmatrix} 2 & 3 \\ 3 & 1 \end{bmatrix}$

- (B)  $\begin{bmatrix} 0.833 & 0.5 \\ 0.5 & 0.667 \end{bmatrix}$
- (D)  $\begin{bmatrix} 0.3636 & -0.2727 \\ -0.2727 & 0.4545 \end{bmatrix}$

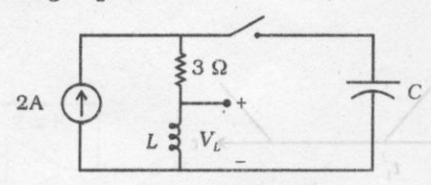44. In the circuit shown, steady state is reached with switch open. The switch is closed at t = 0. At  $t = 0^+$ , the voltage  $V_L$  is,



(A) 0 V

(B) 6 V

(C) - 6V

- (D) 2 V.
- 45. A system function is given by  $\frac{V(s)}{I(s)} = \frac{1}{s+3}$ . If i(t) = u(t) (unit step), v(t) is
  - (A)  $e^{-3}$

(B)  $1 - e^{-3t}$ 

(C)  $1 - 3e^{-3t}$ 

(D)  $\frac{1}{3} - \frac{1}{3}e^{-3t}$ 

Note:

3

at

Please choose to answer part - B below corresponding to your basic degree.

### (E & E : ELECTRICAL AND ELECTRONICS ENGINEERING)

#### SECTION - I

Each question carries one mark.

 $20 \times 1 = 20$ 

- An alternator running at 3000 rpm generates voltage of 50 Hz. The number of poles of the alternator will be the same of the sam

(A) 8 poles (B) 6 poles

(C) 4 poles

- (D) 2 poles.
- Run-away speed of a pelton wheel is

Vol 00001 x (30) X

- (A) full-load speed
- actual speed operating at no-load
- no-load speed when governor mechanism fails
- (D) 80% greater than the normal speed.
- The input-output equation of a 0.5 MW powerhouse is given by  $I = 30 + 0.8L + 0.5L^2$ , 48. where I is in millions of keal per hour and L is in megawatts.

The input when the plant is running at no-load will be

(A) 0.5 kcal/hr

21.3 kcal/hr (B)

(C)  $30 \times 10^6$  kcal/hr


30 kcal/hr. (D)

SPACE FOR ROUGH WORK

[ P.T.O.

- 49. The conductors used for transmitting power must have which of the followin
  - (A) It should have low value of specific resistance
  - (B) It should be light in weight and non-brittle
  - (C) It should have low cost and high tensile strength
  - (D) All of these.
- 50. Ferranti effect on long overhead lines is experienced when
  - (A) the line is lightly loaded
- (B) the power factor is unity
- (C) the power factor is loading
- (D) corona effect is dominant.
- 51. The percentage reactance can be converted into ohmic value with which of the following formulae?
  - (A)  $X_{\text{ohms}} = \frac{X(\%) \times 100 (\text{kV})^2}{\text{kVA}}$
- (B)  $X_{\text{ohms}} = \frac{X(\%) \times 1000 (\text{kV})^2}{\text{kVA}}$
- (C)  $X_{\text{ohms}} = \frac{X(\%) \times (kV)^2}{1000 \text{ (kVA)}}$
- (D)  $X_{\text{ohms}} = \frac{X(\%) \times (10) \times (kV)^2}{kVA}$ .
- 52. For the system shown below the base voltage is,

Transmission line

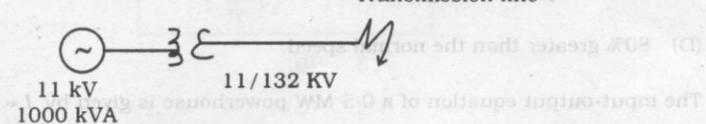

- (A) 11 kV for the system
- (B) 132 kV for the system
- (C) 11 kV for generator and 132 kV for transmission line
- (D) cannot be determined for the given data.

SPACE FOR ROUGH WORK

the no-load losses and measured copper losses are calculated

(C) both the no-load losses and the copper losses are measured

(D) both the no-load losses and the copper-losses are calculated.



[ P.T.O.

- 59. The no-load current of a transformer in terms of full-load current is usually
  - (A) 1% to 3%

(B) 3% to 15%

(C) 9% to 12%

- (D) 12% to 20%.
- 60. The concentric windings are used in core-type transformers with
  - (A) HT winding placed next to core
- (B) LT winding placed next to core
- (C) LT winding on the outer side
- (D) None of these.
- 61. The skin effect increases the effective value of
  - (A) resistance of the conductor
    - (B) reactance of the conductor
    - (C) capacitance of the conductor
    - (D) inductance & capacitance of the conductor.
- 62. The major advantage of a bridge rectifier is that
  - (A) no centre-tap transformer is required
  - (B) the required peak inverse voltage of each diode is double of that for a full-wave rectifier
  - (C) peak inverse voltage of each diode is half of that for a full-wave rectifier
  - (D) the input is more smooth.
- 63. In a thyristor, holding current is
  - (A) more than latching current
- (B) less than latching current
- (C) equal to latching current
- (D) zero.
- 64. The function of snubber circuit connected across an SCR is to
  - (A) suppress dv/dt

(B) increase dv/dt

(C) decrease dv/dt

- (D) none of these.
- 65. For a 3-phase, six-pulse diode rectifier, the average output voltage in terms of maximum value of line voltage  $V_m$  is
  - (A)  $\frac{3\sqrt{2}}{7}$   $V_m$

(B)  $\frac{3 \text{ V}_m}{\pi}$ 

(C)  $\frac{3\sqrt{3}}{2\pi}V_m$ 

(D)  $\frac{3\sqrt{3}}{\pi} V_m.$ 

#### SECTION - II

Each question carries two marks.

 $10 \times 2 = 20$ 

66.	A transformer has a core loss of 64 W and copper loss of 144 W, when it is carrying
	20% overload current. The load at which this transformer will operate at the maximum
	efficiency is

(A) 80%

(B) 66%

(C) 120%

(D) 44%.

67. In a 3-phase star connected alternator a field current of 40 A produces full-load current of 200 A on short circuit and 1160 V an open circuit. If the resistance of the alternator is  $0.5~\Omega$ , then the value of synchronous reactance is

(A) 5.78 Ω

(B) 16·5 Ω

(C) 3·31 Ω

(D) 29 Ω.

68. The forward breakover voltage of a thyristor is 175 volts with a gate pulse of 2 mA. The conduction angle for a sinusoidal voltage of 350 V ( peak ) is

(A) 0°

(B) 30°

(C) 60°

(D) 90°.

69. An SCR can be triggered with a  $\frac{dv}{dt}$  of 200 V/ $\mu$ s. If the charging current flowing through the junction is 5 mA, the equivalent capacitance of depletion layer is

(A) 20 pF

(B) 25 F

(C) 25 pF

(D) 250 pF.

70. A 4-pole lap wound armature has 480 conductors and a flux per pole of 25 mWb. The emf generated when running at 600 rpm, will be

(A) 240 V

(B) 120 V

(C) 60 V

(D) 30 V.

71. Three units of 1:5 transformers are connected in  $\Delta$  – Y to supply a 3-phase load from

			SPACE F	OR ROUGH	MODK	
	(C)	0·306 p.u.	30'0	(D)	0·318 p.u.	
	(A)	0·106 p.u.		(B)	0·206 p.u.	
	30 M	MVA is 0.2 p.u. Th	e p.u. value fo	r the base	values of 13.8 kV	and 50 MVA will be
75.	The	p.u. impedance va	alue of an alte	rnator corr	responding to bas	e values of 13.2 kV and
	(C)	10 A		(D)	20 A.	
	(A)	0 A		(B)	5 A	
	the	anode current will	become			efem) on dynamic
74.	The	anode current th	rough a condu	acting SCR	is 10A. If its gat	te current is made half
	(C)	0.65	contrato toe	(D)	0.55.	(0)
	(A)	0.95		(B)	0.78	
	indi	icates 100 amp an	d the wattmet	er reads 62	kW will be	
73.	The	power factor of	a system on	a 460 V.	3-phase, 60 Hz,	in which the ammete
	(D)	voltage is consta	nt and power i	factor decre	eases.	(C) 3:31 Q
	(C)	voltage decreases	s and power fa	ctor also d	ecreases	
	(B)		somethic realization	a mingel		
	(A)					
			4436 1000			200E (1-10)
72.	A ti				ount of power wh	nose efficiency increase
	(C)			(D)	803 V.	elficitore is consistent
	diggra					rmo beoboye 3°05
	(A)	1000 V		(B)	80 V	

m

es

er

f,

d

(A)

**PWM** 

(C) Delta

#### PART - B

# (E & C and TC : ELECTRONICS & COMMUNICATION ENGINEERING & TELECOMMUNICATION ENGINEERING)

#### SECTION - I

Each question carries one mark.

 $20 \times 1 = 20$ 

For fast switching applications, a power diode should have low on state voltage and low breakdown voltage high on state voltage and high breakdown voltage (C) large reverse recovery time small reverse recovery time. In a single-phase full-wave A.C. voltage controller with R & L load, if  $\beta = 205^{\circ}$  and delay angle  $\alpha = \pi/4$ , then the conduction angle of a thyristor is 280° (A) (B) 220° (C) 60° (D) 160°. The directivity of a broadside array of height 10  $\lambda$  and length 20  $\lambda$  is 34 dB 43 dB 53 dB 35 dB. (C) (D) Which of the following pulse modulation systems is analog? 49.

SPACE FOR ROUGH WORK

(B)

(D)

**PCM** 

Differential delta.

- 50. A signal is defined as x(t) = 4 tri (t). The value of  $x(\frac{1}{4})$  is
  - (A) 4

(B) 3

(C)  $\frac{1}{4}$ 

- (D)  $\frac{1}{3}$ .
- 51. An analog signal is sampled at 36 kHz and quantized into 256 levels. The time duration of a bit of the binary coded signal is
  - (A) 3·47 μs

(B) 2·77 μs

(C) 1.22 µs

- (D) 7.86 μs.
- 52. A coaxial cable having characteristic impedance of 50  $\Omega$  is to feed a half-wave dipole antenna of 75  $\Omega$ . The necessary matching load is
  - (A) 3·33 Ω

(B) 33·3 Ω

(C) 3·3 kΩ

- (D) 33 kΩ.
- 53. The range of firing in case of UJT triggering circuit is
  - (A) 0 90°

(B) 0 - 180°

(C) 0 - 270°

- (D) 0 360°.
- 54. The impulse response h [ n ] of a linear time invariant system is described by  $h[n] = e^{\alpha n} u[n] + e^{\beta n} u[-n]$  where u [ n ] denotes the unit step function and  $\alpha$  &  $\beta$  are constants. The system is stable if
  - (A)  $\alpha$  is positive &  $\beta$  is negative
  - (B)  $\alpha$  is negative &  $\beta$  is negative
  - (C)  $\alpha$  is positive &  $\beta$  is negative
  - (D)  $\alpha$  is negative &  $\beta$  is negative.

- 55. Which of the following is used to download a binary machine program from the development processor's memory into the target processor memory?
  - (A) Device programmers
  - (B) Emulators
  - (C) Debuggers
  - (D) Virtual machines.
- 56. Scaling of channel length by  $\frac{1}{\alpha}$  leads to
  - (A) increase in channel resistance RON
  - (B) decrease in channel resistance RON
  - (C) no change in channel resistance RON
  - (D) infinite value of channel resistance RON.
- 57. Which one of the following is not embedded system characteristic?
  - (A) Single functioned (B)
- (B) Multi-functioned
  - (C) Tightly constrained (D)
    - D) Reactive and real time.
- 58. A thin dipole antenna is  $\frac{\lambda}{15}$ . If its loss resistance is  $1.2 \Omega$  then the efficiency is
  - (A) 41·1%

(B) 59%

(C) 74·5%

- (D) 25·5%.
- 59. For a given data rate, the bandwidth required with *m*-ary transmission is smaller than for binary transmission by
  - (A) log<sub>2</sub>m

(B)  $\frac{\log_2 m}{m}$ 

(C)  $\frac{2}{\log_2 m}$ 

(D)  $\frac{\log_2 m}{2}$ .

(C) t.δ(t)

60.	The	e rms antenna current of an A.	M. tra	ansmitter	increases by	20%	over	the
	uni	nodulated value. The modulation per	centag	e is				-
	(A)	25	(B)	93				
	(C)	47	(D)	16.				
61.	The	e input impedance of a $\frac{\lambda}{8}$ long short	circuit	ed section				
	is							
	(A)	zero	(B)	capaciti	ve amillanimad			
	(C)	inductive	(D)	infinity.	e in channel o			
62.	Wh	ich of the following systems is linear	?					
	(A)	ax [n]+b	(B)	$x^2[n]$				
	(C)	$x[n^2]$	(D)	$e^{x}[n]$ .	e value of chan			
63.	Volt	tage source inverter is used when		is not em				
	(A)	source inductance is small and load	l induc	etance is l	arge			
	(B)	source inductance is large and load	induc	tance is s	mall		(5)	
	(C)	source inductance is large and load	induc	tance is la	arge			
	(D)	source inductance is small and load	l induc	ctance is s				
64.	Stat	tic current is high in						
	(A)	CMOS inverter	(B)	BiCMOS	inverter			
	(C)	NMOS inverter	(D)			t yuani		
65.	The	impulse response of an LTI system is	s u ( t )	. The step	response is			
	(A)	u(t)	(B)	δ(t)				

(D) t.u(t).

e

## SECTION - II

Each question carries two marks.

Given the Z-transform pair 66.

$$3^n n^2 U[n] \stackrel{Z}{\longleftrightarrow} X[Z]$$

the time signal corresponding to  $X[Z^{-1}]$  is

- (A)  $n^2 3^{-n} U[n]$  (B)  $\frac{1}{n^2} 3^{\overline{n}} U[n]$
- (C)  $n^2 3^{-n} U[-n]$

(D)  $\frac{1}{n^2} 3^n U[-n].$ 

Electron transit time is directly proportional to ...... and inversely proportional 67. when it invisions are used to a string to withstand a D.C. voltar will be and

- (A) length,  $V_{ds}$
- the musicuum steady state voltage sharing of each thyristor is 2 kV then the ste
- (C) square of length, V<sub>ds</sub>
- (D)  $E_{ds}$ , length.

A DSB signal is generated using a square law modulator with characteristics  $V_o = A V_i + B V_i^3$ , the output of the non-linear device can be filtered by bandpass filter and the input signal  $V_i = m(t) + \cos(2\pi f_1 t)$ . What is the value of  $f_1$  if the carrier frequency of DSB generator is 1 MHz?

(C) 0.25 MHz

2 MHz.

The antenna is desired to operate on a frequency of 30 MHz whose Q is 40. The 69. bandwidth of the antenna is

(A) 705 kHz

750 kHz

(C) 750 Hz

705 Hz. (D)

70.	The ranges of resistance $R_1 \& I_1$ $V_{BB} = 20 \text{ V}$ , $\eta = 0.66$ , $I_P = 10 \mu\text{A}$ ,		triggering circuit for the parameters: $I_V = 10 \text{ mA}$ are
	(A) $15 \text{ k}\Omega < R_1 < 10 \text{ M}\Omega & 757 \text{ k}$	Ω	
	(B) $5 \text{ k}\Omega < R_1 < 970 \text{ k}\Omega & 7.57 \Omega$	1	[2] X - 2 - [a] U Fir Pe
	(C) $100 \Omega < R_1 < 6800 \Omega & 75.7$	kΩ	X or expansional corresponding to X
	(D) $1.75 \text{ k}\Omega < R_1 < 680 \text{ k}\Omega & 757$	7 Ω.	
71.			nalling at transmission rate of 2400 bps umber of constellation points when data
	(A) 512	(B)	256
e las	(C) 128	(D)	8.4 vilimato si editi tienavi modania
72.			thstand a D.C. voltage of $V_S = 15 \text{ kV}$ and f each thyristor is 2 kV then the steady
	(A) 37·5%	(B)	75%
	(C) 25·15%	(D)	12%.
73.	increasing	on-linear de	reducing and by
	(A) L, W	(B)	W. L
	(C) $V_{ds}, W$	(D)	$V_{ds}, V_{gs}$ .
74.	The second secon	on less than	th 3 kHz. N point is used to compute or equal to 50 Hz. The minimum length
	(A) 0.3 sec	(B)	0.03 sec
	(C) · 0·2 sec	(D)	0·02 sec.
75.	The radiation resistance of an ante		and loss resistance is 8 $\Omega$ . What will be
	(A) 17·78	(B)	17.87
	(C) 17·89	(D)	17.98.

SC

ta

ıd

ly

by

th

bc

#### PART - B

## (BME and ME : BIOMEDICAL ENGINEERING & MEDICAL ELECTRONICS)

#### SECTION - I

Each question carries one mark.  $20 \times 1 = 20$ 

- 46. By definition, ultrasound is sonic energy at frequencies
  - (A) > 20 kHz

< 20 kHz (B)

- (C) ≥ 20 kHz
- (D) ≤ 20 kHz.
- The density of water and most body fluids and tissues is approximately

  - (A)  $2.00 \text{ g/cm}^2$  (B)  $1.00 \text{ g/cm}^2$
  - (C)  $0.5 \text{ g/cm}^2$
- (D)  $0.25 \text{ g/cm}^2$ .
- The frequency range of X-ray is
  - (A) 10<sup>8</sup> MHz 10<sup>10</sup> MHz
- (B)  $10^{10} \text{ MHz} 10^{14} \text{ MHz}$
- (C)  $10^{12}$  MHz  $-10^{16}$  MHz
- (D)  $10^{14} \text{ MHz} 10^{18} \text{ MHz}.$
- In order to visualize gastrointestinal tract during X-ray, barium sulphate is given orally because
  - foreign bodies and bone absorb X-ray images readily than soft tissues
  - (B) to increase X-ray absorption of intestinal tract than surrounding tissue
  - (C) to make intestinal tract empty to enhance visualisation
  - (D). to provide different colours to the intestinal tract to enhance visualisation.
- In which imaging system mathematical reconstruction technique is used to visualise detailed structures of an object?
  - (A) X-ray image intensifier
- (B) CT scanner

(C) MRI system

Ultrasonic imaging system.

51.	When a sequence is circularly shifted in time by 5 units, the magnitude response
	(A) increases by 5 (B) remains unchanged
	(C) remains constant (D) shifts by 5 units.
52.	To detect QRS complex, the ECG is passed through a bandpass filter with a cent
	frequency and a bandwidth of
	(A) 25 Hz, 50 Hz (B) 17 Hz, 50 Hz
	(C) 17 Hz, 6 Hz (D) 25 Hz, 100 Hz.
53.	The transform that is effective in detecting lines in an image is
	(A) Fourier (B) Hough
	(C) Wavelet (D) Hadamard.
54.	The transform used in JPEG image compression is
	(A) Discerete cosine transform • El van X lo agont voltoment off
	(B) Walsh transform
	(C) Hadamard transform
	(D) K.L. transform.
55.	Which of the following filters will in general have best performance in enhancing edg
1	in an image ? I flow mant although segment with X disade anod has atched narrote (/o
	(A) Mean filter (B) Median filter
	(C) Laplace filter (D) Mode filter.
56.	Glass electrode is used to measure/record
	(A) bioelectric potential near within a single cell
	(B) EMG potential from the surface of the skin
	(C) pH of body fluids
16	(D) EEG potential from a local region of the brain.

A) ventricular in the second of the second o	llation fibrillation, artericardiac output is	al fibrillation carried out	and other arrhythm	
B) arrhythmias C) arterial fibri D) ventricular fi Measurement of c A) ultrasound fi B) electromagn C) indicator dil	llation ibrillation, artericardiac output is transmission and etic induction flo	al fibrillation carried out	and other arrhythm	mias. d me avodu
C) arterial fibrical control of the	llation fibrillation, artericardiac output is transmission and	al fibrillation carried out	and other arrhythm	mias. d me avodu
D) ventricular for the desurement of the desurem	ibrillation, artericardiac output is transmission and etic induction flo	al fibrillation carried out deflection management	and other arrhythm	mias. d no avodu
Measurement of (A) ultrasound (B) electromagn	cardiac output is transmission and etic induction flo	carried out	by	
A) ultrasound (B) electromagn (C) indicator dil	transmission and	l reflection mowmeter	nethod	
B) electromagn C) indicator dil	etic induction flo	wmeter		
C) indicator dil				
	ution method	statement suctions		
) thermal con			the daine and its un	
	vection method.	exponential	ad lisw unotverfed hi	
hanges in thr	eshold sensitivi	ity associate	ed with various	middle ear surgica
	e monitored mor	e accurately	using	
) pure tone au	idiometers	(B)	speech audiomete	ers
audiometer	Bekesy	(D)	evoke response au	udiometer system.
he amount of ga	s contained in th	ne lungs at th	ne end of a maximal	inspiration is called
) vital capacit	y golfulovi	(B)	total lung capacity	у
c) inspiratory of	apacity	(D)	forced vital capaci	ity.
hen the signal	and noise spec	tra overlap	techn	ique can separate
epetitive signal fi	om noise withou	it distorting	the signal.	enturnaug siji e i
) bandpass fil	ter	(B)	moving average fil	lter
c) synchronized	daveraging	(D)	notch and comb fi	ilter.
h	vital capacity inspiratory content the signal petitive signal from bandpass filt	vital capacity  inspiratory capacity  hen the signal and noise special petitive signal from noise without bandpass filter  synchronized averaging	ne amount of gas contained in the lungs at the vital capacity (B) inspiratory capacity (D) hen the signal and noise spectra overlap petitive signal from noise without distorting to bandpass filter (B) synchronized averaging (D)	the amount of gas contained in the lungs at the end of a maximal  (B) total lung capacity  (inspiratory capacity  (D) forced vital capacity  then the signal and noise spectra overlap technological technological technological technological from noise without distorting the signal.  (B) moving average file

collegedunia [India's largest Student Review Platform

5000	)		3	2				
62.	The	system is linear if it is						
	(A)	homogeneous		(B)	additive			
	(C)	additive or homogeneous		(D)	additive and homogeneous.			
63.	If th	ne frequency of analog sinusoid is	1 v	vhen s	ampled using sampling frequency			
	abo	ve or below the Nyquist rate, will re	su	lt in di	iscrete time signal that is.			
	(A)	periodic		(B)	aperiodic de la companya de la compa			
	(C)	aliased		(D)	none of these.			
64.	When the system has poles inside the unit circle in $Z$ domain							
	(A)	the system is stable and its impul	se	respor	nse is a decaying function			
	(B)	time domain behaviour will be exp	or	ential	ly rising signal			
	(C)	the system is unstable						
	(D)	the impulse response is marginally	y c	onstar	nt.			
65.	Mul	tiplication in frequency domain is c	on	volutio	on in time domain. It is a			
	(A)	linear convolution			E ESTABLISHMENT SINCE AND THE			
	(B)	circular convolution						
	(C)	any type of convolution			the autount of Eas continued in th			
	(D)	linear convolution converted to cir	cu	lar cor	nvolution.			
		SECT	ric	ON – II				
		Each question	ca	rries tu	wo marks. The land 10 × 2			
66.		minimum sampling rate required to its samples is	to	recons				
	(A)	500		(B)	1000			
	(C)	2000		(D)	4000.			
		SPACE FOR	R	OUGH	WORK			





her

20

: ) t

- Speech is digitized using a sampling rate of 8 kHz. An antialiasing filter with cut-off frequency of 3.4 kHz is preceded by sampler. The loss of speech signals in the frequency range 3.4 20 kHz due to antialiasing filter introduces a degradation in the signal quality. On the other hand, sampling without antialiasing filter also introduces degradation in the signal quality. Which of the following statements is true?
  - (A) Degradation with antialiasing filter is less
  - (B) Degradation without antialiasing filter is less
  - (C) Degradation with or without antialiasing filter is the same
  - (D) Degradation with antialiasing filter in the above frequency band is not much important.
- 68. The 2D DFT of the image  $\begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$  is
  - (A)  $\begin{bmatrix} 4 & 0 \\ 0 & 0 \end{bmatrix}$

(B)  $\begin{bmatrix} 0 & 4 \\ 0 & 0 \end{bmatrix}$ 

(C)  $\begin{bmatrix} 0 & 0 \\ 4 & 0 \end{bmatrix}$ 

- (D)  $\begin{bmatrix} 0 & 0 \\ 0 & 4 \end{bmatrix}$
- 69. The total number of bits required to represent a 256 ×256 image with 256 gray level is
  - (A) 524268

(B) 65536

(C) 16777216

- (D) 131072.
- 70. An ECG signal contains combination of base line drift, high frequency noise and power line and its harmonics interference. Which combination of filters are required?
  - (A) LP filter, HP filter and Notch filter
  - (B) LP filter and Comb filter
  - (C) LP filter, HP filter and Comb filter
  - (D) LP filter, HP filter and BR filter.

71.	according to their frequency of occurrence. Data that occur frequently are assign shorter code words.				
	(A)		B)	Adaptive coding	
	(C)	Runlength coding (	D) .	AZTEC coding.	
72.	The number of stages of FET computations required for the computation of DFT of 5 point sequence is				
	(A)	0	D)	Q	
	(C)	7	D)	100 the state of the southbarged (0) .	
73.	Which of the following properties are true for an IIR filter designed using biline transformation method ?				
		I) Requires the use of antialiasing i	filter		
		II) Requires prewrapping the filter cut-off frequencies			
		III) Not suited for the design of HP fi	lters		
		IV) Result in unique mapping from analog to digital frequencies.			
	(A)	I & II	B)	I & III	
	(C)	II & III	D)	II & IV. and to reduce the later of	
74.	The number of multiplications required for performing the convolution of sequences with identical length and using direct method is				
	(A)	256	B)	120	
	(C)	128	D)	64.	
75.	The residue method evaluates the residue of the function at poles that are				
	(A)	outside the closed contour in the ROC	;	(A) LP PART HIR GHET AND TAIL	
	(B)	anywhere in ROC		(B) . LP filler, and Comb filler	
	(C)	(C) inside the closed contour in the ROC			
	(D)	outside the ROC.	lteral	(D) LP filter, MP filter and (BB)	



# farigle blocking come me PART - B a at ( no ) A lamara and atargets A (IT: INSTRUMENTATION TECHNOLOGY) SECTION - I

Each question carries one mark.

12

3

ice

led

(C) Xi-alla lor all a cod Xi-alla Xi milor all a resi 46. The numerical aperture of the fibre is expressed as

- (A)  $(n_1 n_2)^{\frac{1}{2}}$  (B)  $(n_1^2 n_2^2)^{\frac{1}{2}}$
- (C)  $(n_2 n_1)_2^1$  (D)  $(n_2^2 n_1^2)_2^1$

ear

wo

Linearity of a transducer is often specified in terms of

- (A) percentage of linearity
- percentage of non-linearity (B)

kagmanashan (3) \*

- (C) percentage of maximum error (D) percentage of error.

Bioelectric potentials are generated due to difference in concentration of 48.

(A) Na+, Cl- & K+

Na<sup>+</sup>, Cl<sup>-</sup> & Mg<sup>+</sup> (B)

- (C) Na<sup>+</sup>, Cl<sup>-</sup> & Ca<sup>+</sup> (D) Ca<sup>+</sup>, Mg<sup>+</sup> & Cl<sup>-</sup>.

49. Which of the following is called as the natural pacemaker of the heart?

- (A) AV node (B) Bundle of Nis
- (C) SA node

Purkinje fibres. (D)

50. The CO<sub>2</sub> laser emits radiation at the wavelength of

(A) 1.06 μm

325 nm (B)

(C)  $2.36 - 3 \mu m$ 

(D) 10.6 µm.

51. Which of the following represents the impulse response of a system defined by  $H(z) = z^{-m} ?$ 

- (A) u[n-m] (B)  $\delta[n-m]$

- (C)  $\delta[m]$  (D)  $\delta[m-n]$ .

x(t) or x(n) is defined to be a power signal, if and only if the average power content of the signal is a/an

- (A) finite quantity and all power signals will have  $E=\infty$
- (B) infinite quantity and all power signals will have  $E = \infty$
- infinite quantity and all power signals will have E = 0
- infinite quantity and all power signals will have E = 0.

- A discrete time signal X (n) is said to be an even and odd signal if it satisfies condition
  - (A) X[-n] = X[n] for all n and X[-n] = -X[n] for all n respectively
  - (B) X[-n] = -X[n] for all n and X[-n] = X[n] for all n respectively
  - (C) X[-n] = X[n] for all n and X[-n] = X[n] for all n respectively
  - (D) none of these.
- A continuous time signal X(t) is said to be periodic with period T, if there is a
  - negative non-zero value of T for which X(t+T) = X(T) for all t
  - positive non-zero value of T for which X(t+T) = X(T) for all t
  - (C) negative non-zero value of T for which X(t+T) = X(t) for all t
  - positive non-zero value of T for which X(t+T) = X(t) for all t.
- A continuous time LTI system is represented by the impulse response  $h(t) = e^{-3t}$ 55. The system is
  - (A) unstable and causal
- stable and non-causal (B)
- stable and causal (D)
  - unstable and non-causal.
- The value of damping ratio is determined using  $\zeta$ . ... If  $0 < \zeta < 1$  then the system 56. to be
  - (A) overdamped

critically damped (B)

underdamped

- undamped. (D)
- Gross errors are mainly due to
  - instrumental errors (A)

- (B) unknown causes
- environmental errors
- (D) human errors.
- The resistance of thermistor at temperature *T* is given by 58.
  - (A)  $R_t = R_o \exp \left[\beta \left(T_o T\right) / T T_o\right]$  (B)  $R_t = R_o \exp \left[\left(T_o T\right) / T T_o\right]$
  - (C)  $R_t = R_o \exp \left[\beta (T T_o)\right]$
- (D)  $R_t = R_o \exp \left[\beta \left(T T_o\right) / TT_o\right].$
- Typical operating excitation of linear variable differential transformer ( LVDT ) is 59.
  - (A) 6 V at 2.5 kHz
- (B) 5 V at 2.5 kHz
- (C) 6 V at 5 kHz
- (D) 5 V at 5 kHz.

s the 60. Film Gamma of an X-ray film is expressed as

(A) 
$$\gamma = \frac{D_1 - D_2}{\log_{10} E_2 - \log_{10} E_1}$$

(B) 
$$\gamma = \frac{D_1 - D_2}{\log_{10} E_1 - \log_{10} E_2}$$

(C) 
$$\gamma = \frac{D_2 - D_1}{\log_{10} E_2 - \log_{10} E_1}$$

(D) 
$$\gamma = \frac{D_2 - D_1}{\log_{10} E_1 - \log_{10} E_2}$$


Blood gas analysers are designed to measure

(A) pH

pH and pCO<sub>2</sub> (B)

(C) pCO<sub>2</sub> and pO<sub>2</sub>

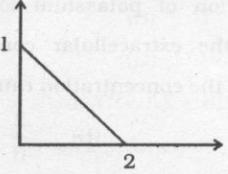
- (D) pH,  $pCO_2$  and  $pO_2$ .
- Identify the correct Laplace transform for the signal given in figure :



(t-1).

- (A)  $\frac{1}{T_2^2} \left[ 1 e^{-TS} \left( 1 + TS \right) \right]$
- (B)  $\frac{1}{T_2^2} \left[ e^{-TS} \left( 1 + TS \right) \right]$
- (C)  $\frac{1}{T_0^2} \left[ e^{-TS} + (1 TS) \right]$  (D)  $\frac{1}{T_0^2} \left[ 1 e^{-TS} + TS \right]$ .

The function of the following circuit is

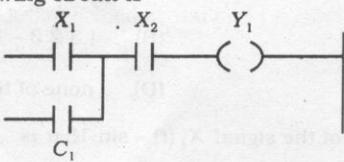

- (A)  $Y_1 = (X_1 \text{ OR } C_1) \text{ AND } X_2$
- (B)  $Y_1 = (X_1 \text{ OR (NOT } C_1)) \text{ AND } X_2$
- (C)  $Y_1 = (X_1 \text{ AND } X_2) \text{ OR } C_1$
- (D)  $Y_1 = (X_1 \text{ AND } X_2) \text{ OR (NOT } C_1).$

The transfer function of Tachometer is of the form

(A) KS

(D)  $\frac{K}{S(S+1)}$ .

The thermocouple used for temperature measurement may have

only one junction

two junctions (B)

2 to 20 junctions

no junction. (D)

#### SECTION - II

Each question carries two marks.

 $10 \times 2 = 20$ 

- 66. What is the output voltage of a transducer which has the excitation potential of 5 V D.C, applied force 15 g and a sensitivity of 10  $\mu$  V/V-g?
  - (A) 750 mV

(B) 750 μV

(C) 7.5 V

- (D) 75 V.
- 67. The intracellular concentration of potassium ions in a group of cells averages  $150\times10^{-6}~\text{moles/cm}^3$  and the extracellular concentration of potassium averages  $6\times10^{-6}~\text{moles/cm}^3$ . What is the concentration ratio ?
  - (A)  $\frac{1}{4}$

(B)  $\frac{2}{6}$ 

- (C)  $\frac{1}{8}$
- $[(27+1)^{\frac{1}{2}}] = [(27+1)^{\frac{1}{2}} = -1]$
- 68. Let two signals be  $X_1(n) = \begin{bmatrix} 1 & 2 & -1 & 2 \end{bmatrix}$  and  $X_2(n) = \begin{bmatrix} -2 & 1 & 3 & 1 \end{bmatrix}$  and the addition of these two signals Y(n) be equal to
  - (A) [-1323]

(B) [323-1]

(C) [3-132]

- (D) none of these.
- 69. The fundamental period of the signal  $X_1(t) = \sin 15\pi t$  is
  - (A) 0.13333 second

(B) 1.3333 seconds

(C) 13.333 seconds

- (D) 0.013333 second.
- 70. The equation for critical damping is
  - (A)  $B = x(0) + \omega_0 x(0)$

- (B)  $B = \frac{-\gamma + x(0) x(0)}{\gamma - \gamma +}$
- (C)  $B = \frac{1}{\omega d} \left( \zeta \omega_0 \ x(0) + \dot{x}(0) \right)$
- (D) none of these.

V

S

:S

of

71.  $\oint f_1(t) = 4$  for 0 < t < 2

= 0, otherwise

 $f_2(t) = u(t-1)$  the convolution is  $f = f_1 \times f_2$ . The value of  $f_3(t)$  is

(A) 0

(B)

(C) 8

12. (D)

A resistance strain gauge has a gauge factor of 2. The change in resistance  $\Delta R$ , of the strain gauge element due to applied stress ( Assume strain (  $\sigma$  ) =  $5 \times 10^{-4}$  ) is

0.001%

(B) 0.01%

(C) 0·1%

(D) 1%.

A system described by state equation  $X^1 = AX + BU$ . The O/P is given by Y = CX where  $A = \begin{bmatrix} -4 & -1 \\ 3 & -1 \end{bmatrix}, B = \begin{bmatrix} 1 \\ 1 \end{bmatrix}, C = \begin{bmatrix} 1 & 0 \end{bmatrix}$ . Transfer function (TF) G(S) of system is

(A)  $\frac{S}{S^2 + 5S + 7}$ 

(C)  $\frac{S}{S^2 + 3S + 2}$ 

(B)  $\frac{1}{S^2 + 5S + 7}$ (D)  $\frac{1}{S^2 + 3S + 2}$ 

74. Let X(n) = n;  $-3 \le n \le 3$ . The folded signal of X(n) will be equal to

- (A)  $X_1(n) = -X(-n) = n; -3 \le n \le 3$
- (B)  $X_1(n) = X(-n) = -n + 1; -3 \le n \le 3$
- (C)  $X_1(n) = X(-n) = -n 1; -3 \le n \le 3$
- (D)  $X_1(n) = X(-n) = -n; -3 \le n \le 3.$

The impulse response of an LTI system is  $e^{-2t}$ . If the input is a unit step with system initially at rest, the response is given by

(A)  $1 - e^{-2t}$ 

(B)  $\frac{1}{2} - \frac{1}{2}e^{-2t}$ 

(C)  $\frac{1}{2} + \frac{1}{2}e^{-2t}$ 

(D)  $-2e^{-2t}$ .