
#### **Basic Electrical Engineering**

| 1. | An emf of 8V is induced in a coil of inductance 4H. The rate of change of current | ( |  |
|----|---|---|--|
|    | must be   |   |  |
|    | (a) 32 A/sec  |   |  |
|    | (b) 0.5 A/sec   |   |  |
|    | (c) 2A/sec  |   |  |
|    | (d) 1 A/sec   |   |  |
| 2. | Two coils have self inductance of 5H and 1H, the mutual inductance being zero. If | ( |  |
|    | the two coils are connected in series, ,the total inductance will be              |   |  |
|    | (a) 4H  |   |  |
|    | (b) 5H  |   |  |
|    | (c) 3H  |   |  |
|    | (d) 6H  |   |  |
| 3. | Four resistors 5 Ohm, 10 Ohm, 20 Ohm, and 40 Ohm, are connected in parallel       | ( |  |
|    | across 20V battery. The highest power will be dissipated in                       |   |  |
|    | (a) 5 Ohm   |   |  |
|    | (b) 10 Ohm  |   |  |
|    | (c) 20 Ohm  |   |  |
|    | (d) 40 Ohm  |   |  |
| 4. | Two inductors carrying current in opposite direction are connected in series. The | ( |  |
|    | total inductance is   |   |  |
|    | (a) $L_1 + L_2 + 2M$  |   |  |
|    | (b) $L_1 + L_2 - 2M$  |   |  |
|    | (c) $\frac{L_1L_2-M^2}{L_1+L_2+2M}$   |   |  |
|    | $L_1 + L_2 + 2M$ $L_1 L_2 - M^2$  |   |  |
|    | (d) $\frac{-\frac{1}{L_1+L_2}-\frac{1}{2M}}{\frac{1}{L_1+L_2}-\frac{1}{2M}}$      |   |  |
| _  | ent lain the circuit g  | , |  |
| 5. | The current I₀ in the circuit given below will be                                 | ( |  |
|    |   |   |  |
|    | → 1 <sub>0</sub>  |   |  |
|    | ±++++++++++++++++++++++++++++++++++++   |   |  |
|    | $\frac{100}{2}$   |   |  |
|    |   |   |  |
|    |   |   |  |
|    | (a) 4 A   |   |  |
|    | (b) 7.5 A   |   |  |
|    | (c) 10 A  |   |  |
| _  | (d) 15 A  |   |  |
| 6. | A constant current of 5mA charges a 10 μF capacitor for 1sec. The voltage across  | ( |  |
|    | the capacitor is  |   |  |
|    | (a) 50V   |   |  |
|    | (b) 250V  |   |  |
|    | (c) 500V  |   |  |
| 7  | (d) 1000V The direction of the induced emf is found by                            | , |  |
| 7. | The direction of the induced emf is found by                                      | ( |  |
|    | (a) Fleming's right hand rule   |   |  |

|     | (b) Lenz's law   |   |   |
|-----|--|---|---|
|     | (c) Fleming's left hand rule   |   |   |
| 8.  | (d) Biot-savart law The angular velocity of a sine wave of 50Hz is                           | 1 | ١ |
| ο.  | (a) $50\pi$  | ( | , |
|     | (a) 30π<br>(b) 100π  |   |   |
|     | (c) $\pi/50$   |   |   |
|     | (d) $\pi/150$  |   |   |
| 9.  | A 1.2 V , 2400 mAh battery connected to a 10 Ohm resistor will be                            | ( | ) |
|     | completely discharged by the end of  |   |   |
|     | (a) 10 hours   |   |   |
|     | (b) 1 hour   |   |   |
|     | (c) 12 hours   |   |   |
|     | (d) 21 hours   | , |   |
| 10. | An alternating current has a peak value of 2A. If its peak factor is $\sqrt{2}$ and its form | ( | ) |
|     | factor is $\frac{\pi}{2\sqrt{2}}$ , its average value is                                     |   |   |
|     |  |   |   |
|     | (a) $\frac{8}{\pi}A$   |   |   |
|     | n.   |   |   |
|     | (b) $\frac{4}{\pi}A$   |   |   |
|     | $\tau$ $\pi$   |   |   |
|     |  |   |   |
|     | (c) $\frac{\pi}{4}A$   |   |   |
|     | Ī  |   |   |
|     | (d) $\frac{\pi}{2}A$   |   |   |
| 11. | (Er 13010  | 1 | ١ |
| 11. |  | ( | , |
|     | (a) $\frac{R}{\sqrt{R^2 + X^2}}$   |   |   |
|     | (b) $\frac{X}{R^2 + X^2}$  |   |   |
|     | (c) $\frac{R^2 - \frac{R}{X^2}}{X}$  |   |   |
|     | (d) $\frac{R}{\sqrt{R}} \frac{Y}{2} \frac{X}{2}$   |   |   |
| 12  |  | , | ١ |
| 12. | 119  | ( | ) |
|     |  |   |   |
|     | <u></u>  |   |   |
|     | 3 6  |   |   |
|     | (a) 6  |   |   |
|     | (b) 4.5  |   |   |
|     | (c) 3  |   |   |
| 13. | (d) 11 The $X_L$ offered by an inductance of 1H to a current $I_mSin10\pi t$ is              | , | ١ |
| 13. | (a) $100 \Omega$   | ( | , |
|     | (a) 100 Ω<br>(b) 50 Ω  |   |   |
|     | (b) 30 Ω<br>(c) 31.4 Ω   |   |   |
|     | (d) 314 Ω  |   |   |
| 14. | In a R-L-C circuits, $v(t)=20 \sin(314t+5\pi/6)$ and $i(t)=10 \sin(314t+2\pi/3)$ . The power | ( | ) |
|     | ·  |   |   |

|     | factor of the circuit is  |   |   |
|-----|---|---|---|
|     | (a) 0.5 lead  |   |   |
|     | (b) 0.866 lag   |   |   |
|     | (c) 0.866 lead  |   |   |
|     | (d) 0.5 lag   |   |   |
| 15. | The device which recovers a part of heat from the flue gases is   | ( | ) |
|     | (a) Condenser   |   |   |
|     | (b) Evaporator  |   |   |
|     | (c) Draft tube  |   |   |
|     | (d) Economiser  |   |   |
| 16. | Steam power plants work closely on  | ( | ) |
|     | (a) Binary vapour cycle   |   |   |
|     | (b) Bragtn cycle  |   |   |
|     | (c) Rankine cycle   |   |   |
|     | (d) Carnot cycle  |   |   |
| 17. | Ash handling plant is located in between  | ( | ) |
|     | (a) Boiler & Ash storage  |   |   |
|     | (b) Boiler & Chimney  |   |   |
|     | (c) Boiler & Super heater   |   |   |
|     | (d) Boiler & Coal storage   |   |   |
| 18. | The electrical by the control of the electric plant in kW is given by the   | ( | ) |
|     | expression  | • | , |
|     | (a) $N_S = N.\sqrt{P}/H^{0.75}$   |   |   |
|     | (b) $N_c = \sqrt{N} \cdot P/H^{3/2}$  |   |   |
|     | (b) $N_s \equiv \sqrt{N} \cdot P/H\hat{3}/2$<br>(c) $N_s = N \cdot \sqrt{P}/H_{1.25}$<br>(d) $N_s = N \cdot \sqrt{P}/H_{2/3}$ |   |   |
|     | $\begin{pmatrix} C \\ A \end{pmatrix} \stackrel{N_s}{\sim} = N \cdot \sqrt{P} / H_{2/3}$                                      |   |   |
| 10  | (u) e_head in mete  | , | ١ |
| 19. | If H is the head in meters, $w$ is the specific gravity in Kg/m³, Q is discharge in   | ( | ) |
|     | m³/sec and η is efficiency then power output of Hydro Electric Plant is   |   |   |
|     | (a) $\frac{WQH}{\eta}$  |   |   |
|     | (b) $\frac{w\dot{Q}}{H} X \eta$   |   |   |
|     | (a) WOHX n  |   |   |
|     | (c) $\psi QHX \eta$<br>(d) $\frac{\partial H}{\partial w}X\eta$   |   |   |
|     | (d) -w  |   |   |
| 20. | Control rods for nuclear reactor are made of  | ( | ) |
|     | (a) Graphite  |   |   |
|     | (b) Cadmium   |   |   |
|     | (c) Concrete  |   |   |
|     | (d) Lead  |   |   |
| 21. | Which of the following material is used a moderator   | ( | ) |
|     | (a) Graphite  |   |   |
|     | (b) Boron   |   |   |
|     | (c) N <sub>a</sub> k liquid   |   |   |
|     | (d) Plutonium   |   |   |
| 22. | The equivalent resistance of a transformer referred to secondary is given by  | ( | ) |
|     | (a) $r_1 + r_2 \left(\frac{N_1}{N_3}\right)^2$  |   |   |
|     | (b) $r_2 + r_1 \left( \frac{N_1}{N_2} \right)^2$  |   |   |

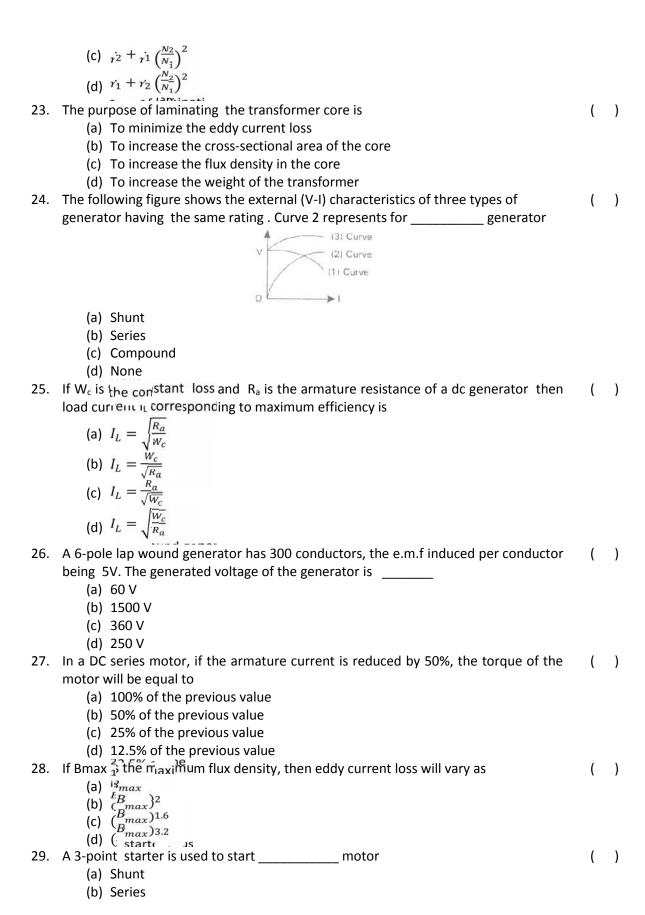

|     | (c) Compound  |   |   |
|-----|---|---|---|
| 20  | (d) Differential compound   | , | , |
| 30. | 1 07  | ( | ) |
|     | (a) Three phase balanced energy only  |   |   |
|     | (b) Three phase unbalanced energy only  |   |   |
|     | (c) Both (a) and (b)  |   |   |
| 24  | (d) Two phase energy  | , | , |
| 31. | To measure insulation resistance of insulators, the instrument required is          | ( | ) |
|     | (a) Ohm meter   |   |   |
|     | (b) Meggar  |   |   |
|     | (c) Ammeter   |   |   |
|     | (d) Voltmeter   |   | , |
| 32. |   | ( | ) |
|     | series, then the amount of current flow in an external resistance of R ohms will be |   |   |
|     | equal to  |   |   |
|     | (a) $\frac{nE}{R}$  |   |   |
|     | (b) $\frac{nE}{B+r}$  |   |   |
|     | nE  |   |   |
|     | (C) $\frac{R+nr}{nF}$   |   |   |
|     | (d) used for I  |   |   |
| 33. |   | ( | ) |
|     | 1. Soldering iron 2. Blow lamp 3. Ladle 4. Pot                                      |   |   |
|     | (a) 1   |   |   |
|     | (b) 2,3,4   |   |   |
|     | (c) 1,2,3,4   |   |   |
|     | (d) 2,3   |   |   |
| 34. | In concealed conduit wiring, the switches used are                                  | ( | ) |
|     | (a) Flush switches  |   |   |
|     | (b) Tumbler switches  |   |   |
|     | (c) Knife switches  |   |   |
|     | (d) Iron clad switches  |   |   |
| 35. | Lakin Hickey is used to   | ( | ) |
|     | (a) Cut the metal   |   |   |
|     | (b) Make holes in wood  |   |   |
|     | (c) Fixing conduit  |   |   |
|     | (d) Bending conduit   |   |   |
| 36. | The most economical wiring used in public buildings is                              | ( | ) |
|     | (a) C.T.S wiring  |   |   |
|     | (b) Conduit wiring  |   |   |
|     | (c) Casing and capping wiring   |   |   |
|     | (d) None  |   |   |
| 37. |   | ( | ) |
|     | (a) Element rating / Minimum fusing current   |   |   |
|     | (b) Minimum fusing current / Element rating   |   |   |
|     | (c) Element rating  |   |   |
|     | (d) None  |   |   |
| 38. |   | ( | ) |
|     | (a) ½ m²c   |   |   |

|     | (b) ½ mc <sup>2</sup>                                |   |   |
|-----|--|---|---|
|     | (c) $\frac{1}{2}$ cv <sup>2</sup>                    |   |   |
|     | (d) mc <sup>2</sup>                                  |   |   |
| 39. | The function of a dry cell is to convert:            | ( | ) |
|     | (a) chemical energy to mechanical energy             |   |   |
|     | (b) chemical energy to electrical energy             |   |   |
|     | (c) electrical energy into mechanical energy         |   |   |
|     | (d) electrical energy into magnetic energy           |   |   |
| 40. | Distilled water is used in electrolytes because it : | ( | ) |
|     | (a) prevents or slows down local action              |   |   |
|     | (b) speeds up electrochemical action                 |   |   |
|     | (c) improves specific gravity                        |   |   |
|     | (d) prevents polarization                            |   |   |

| SR NO | KEY    |
|-------|--------|
| 1     | С      |
| 2     | D      |
| 3     | Α      |
| 4     | В      |
| 5     | D      |
| 6     | С      |
| 7     | A,B    |
| 8     | В      |
| 9     | D      |
| 10    | В      |
| 11    | Α      |
| 12    | D      |
| 13    | С      |
| 14    |        |
| 15    | B<br>D |
| 16    | С      |
| 17    | А      |
| 18    | С      |
| 19    | С      |
| 20    | В      |
| 21    | Α      |
| 22    | С      |
| 23    | Α      |
| 24    | В      |
| 25    | D      |
| 26    | D      |
| 27    | С      |
| 28    | В      |
| 29    | Α      |
| 30    | С      |
| 31    | В      |
| 32    | С      |
| 33    | В      |
| 34    | Α      |
| 35    | D      |
| 36    | В      |
| 37    | В      |
| 38    | D      |
| 39    | В      |
| 40    | Α      |