#### POST GRADUATE COMMON ENTRANCE TEST-2018

DATE and TIME		COURSE		SUBJECT	
14-07-2018 2.30 p.m. to 4.30 p.m.	cou	M.Tech/M.Arch/ rses offered by UVCE/UBDTCE		ELECTRICAL SCIENCES (E&E/E&C/TC/BME&ME/IT)	
MAXIMUM MARKS	TOTAL DURATION 150 Minutes		MAXIM	UM TIME FOR ANSWERING	
100			120 Minutes		
MENTION YOUR PG	CET NO.	Q	UESTION	BOOKLET DETAILS	
		VERSION	CODE	SERIAL NUMBER	
		A		163205	

DOs:

- Candidate must verify that the PGCET number & Name printed on the OMR Answer Sheet is tallying with the PGCET number and Name printed on the Admission Ticket. Discrepancy if any, report to invigilator.
- 2. This question booklet is issued to you by the invigilator after the 2<sup>nd</sup> bell i.e., after 2.25 p.m.
- The Version Code of this Question Booklet should be entered on the OMR Answer Sheet and the respective circle should also be shaded completely.
- The Version Code and Serial Number of this question booklet should be entered on the Nominal Roll without any mistakes.
- 5. Compulsorily sign at the bottom portion of the OMR answer sheet in the space provided.

DON'Ts:

- 1. The timing and marks printed on the OMR answer sheet should not be damaged / mutilated / spoiled.
- The 3<sup>rd</sup> Bell rings at 2.30 p.m., till then;
  - Do not remove the paper seal / polythene bag present on the right hand side of this question booklet.
  - Do not look inside this question booklet.
  - Do not start answering on the OMR answer sheet.

#### IMPORTANT INSTRUCTIONS TO CANDIDATES

- This question booklet contains 75 (items) questions and each question will have one statement and four answers.
   (Four different options / responses.)
- After the 3<sup>rd</sup> Bell is rung at 2.30 p.m., remove the paper seal / polythene bag on the right hand side of this
  question booklet and check that this booklet does not have any unprinted or torn or missing pages or items etc.,
  if so, get it replaced by a complete test booklet. Read each item and start answering on the OMR answer sheet.
  - During the subsequent 120 minutes:
    Read each question (item) carefully.
  - Choose one correct answer from out of the four available responses (options / choices) given under
    each question / item. In case you feel that there is more than one correct response, mark the response
    which you consider the best. In any case, choose only one response for each item.
  - Completely darken / shade the relevant circle with a BLUE OR BLACK INK BALLPOINT PEN against the question number on the OMR answer sheet.

ಸರಿಯಾದ ಕ್ರಮ	ತನ್ನು ಕ್ರಮಗಳು WRONG METHODS				
CORRECT METHOI					
A • © •					


- Use the space provided on each page of the question booklet for Rough Work. Do not use the OMR answer sheet for the same.
- After the last Bell is rung at 4.30 p.m., stop marking on the OMR answer sheet and affix your left hand thumb impression on the OMR answer sheet as per the instructions.
- 6. Handover the OMR ANSWER SHEET to the room invigilator as it is.
- After separating the top sheet (KEA copy), the invigilator will return the bottom sheet replica (Candidate's copy)
  to you to carry home for self-evaluation.
- 8. Preserve the replica of the OMR answer sheet for a minimum period of ONE year.
- 9. Only Non-programmable calculators are allowed.

**Marks Distribution** 

PART-A : (Section 1) 30 Questions :  $30 \times 1 = 30$  (Section 2) 15 Questions :  $15 \times 2 = 30$ PART-B : (Section 1) 20 Questions :  $20 \times 1 = 20$  (Section 2) 10 Questions :  $10 \times 2 = 20$ 

EE-A



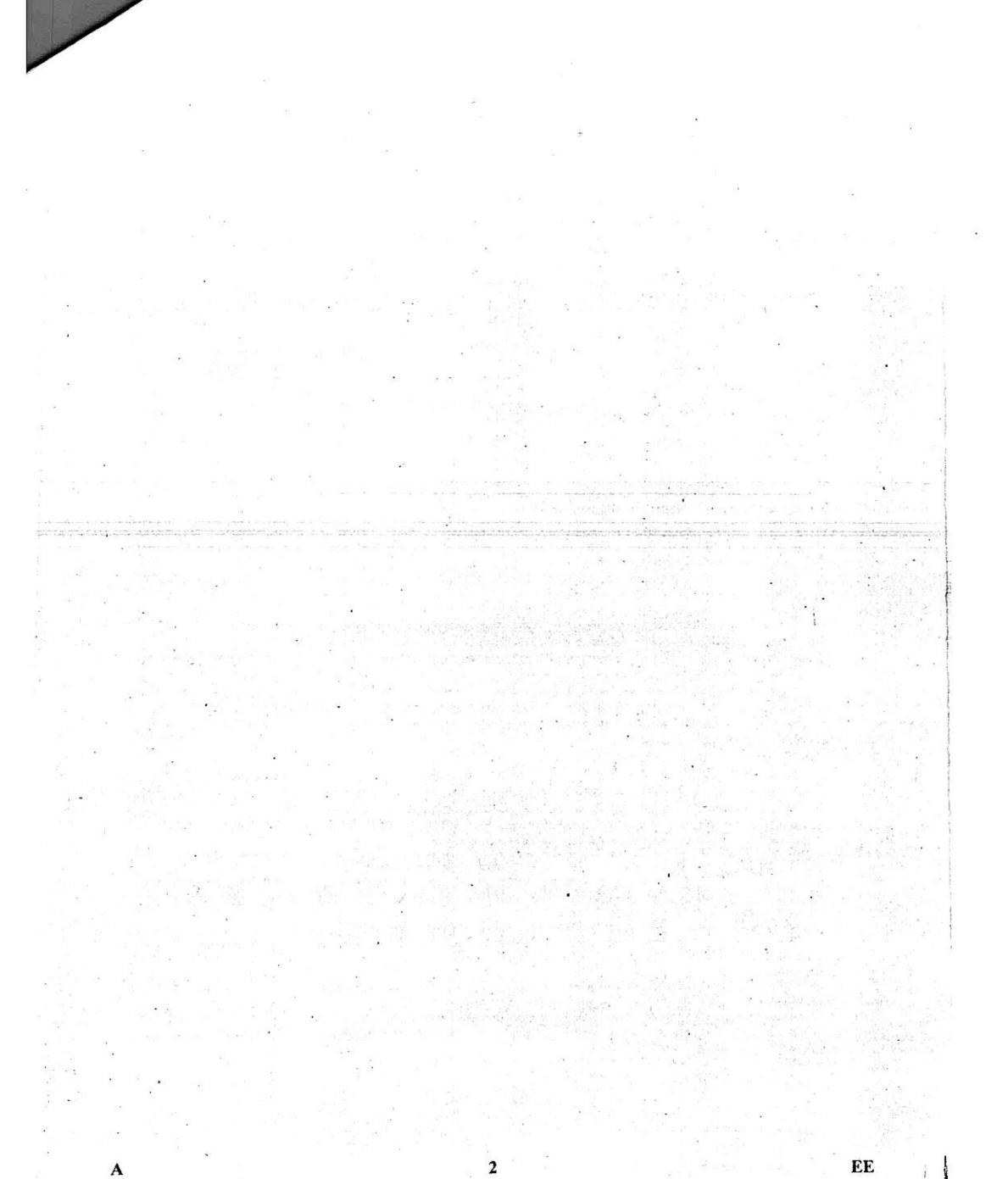



# (Common to E & E / E & C / TC / BME & ME / IT)

#### PART - A (SECTION - I)

#### Each question carries one mark.


 $(30 \times 1 = 30)$ 

- Maximal directional derivative of  $\phi = x + y + z$  at (1, 2, 3) is
  - (A)  $-\sqrt{3}$

- (D) −3
- $\lim_{x \to 2} \left[ \frac{2^x 4}{x 2} \right]$ is
  - $(A) log_e 2$
- (B)  $\log_e 4$
- $(C) log_e 8$
- (D)  $\log_e 16$
- For independent events A and B with P(A) = 0.3, P(B) = 0.2, then  $P(A \cup B)$  is
  - (A) 0.44
- (B) 0.4
- (C) 0.55
- (D) 0.5
- Standard form of one-dimensional wave equation is

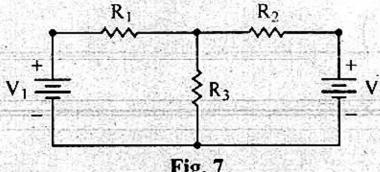  - (A)  $C^2 \frac{\partial^2 u}{\partial x^2} = \frac{\partial u}{\partial t}$  (B)  $C^2 \frac{\partial u}{\partial x} = \frac{\partial^2 u}{\partial t^2}$
  - (C)  $C^2 \frac{\partial^2 u}{\partial x^2} = \frac{\partial^2 u}{\partial t^2}$  (D)  $C^2 \frac{\partial u}{\partial x} = \frac{\partial u}{\partial t}$
- (B)
- (D)  $\frac{3}{7}$

- In Poisson distribution, mean and standard deviation respectively are
  - (A) np & np
  - (B) np & $\sqrt{np}$
  - (C)  $np \& n^2p^2$
  - (D)  $n^2p^2$ & np
- In the circuit shown in Fig. 7, the number of nodes is



- Fig. 7
- (B) two
- three

one

- (D) four
- The circuit shown in Fig. 7 has branches.
  - (A) two
  - four (B)
  - three
  - (D) None of these .
- The superposition theorem is used when the circuit contains
  - (A) a single voltage source
  - number of voltage sources (B)
  - passive elements only (C)
  - none of the above (D)

 In the Fig. 10 shown the value of Thevenin's voltage E<sub>TH</sub> is


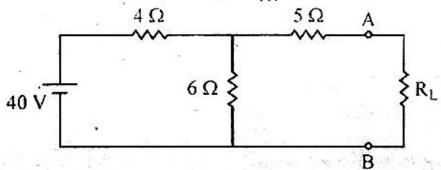



Fig. 10

- (A) 20 V
- (B) 24 V
- (C) 12 V
- (D) 36 V
- 11. Divergence of gradient of scalar potential V is
  - (A)  $\nabla . \nabla V = 0$
- (B)  $\nabla . \nabla V = \nabla V^2$
- (C)  $\nabla . \nabla V = \nabla^2 V$
- (D)  $\nabla . \nabla V = 1$
- 12. Electric flux density D for a metallic surface having surface charge density  $\rho_s$  c/m<sup>2</sup> is
  - (A)  $D = \rho_s$
- (B)  $D = 2 \rho_s$
- (C) D=0
- (D)  $D = \rho_s/2$
- 13. Maximum efficiency of a Class-B power amplifier is
  - (A) 25%
- (B) 50%
- (C) 78.54%
- (D) 90%
- 14. The gain bandwidth product of a two stage CE amplifier is
  - (A) greater than that of one stage
  - (B) less than that of one stage.
  - (C) same as that of one stage.
  - (D) product of the two gain bandwidth products of each stage.

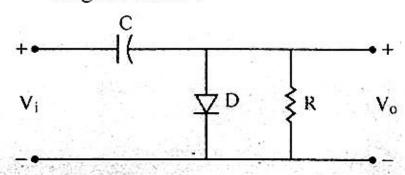15. What is the circuit in the given diagram called?



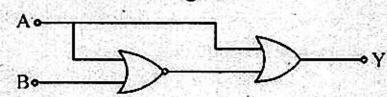- (A) Clipper
- (B) Clamper
- (C) Rectifier
- (D) Lowpass filter
- **16.** Convert  $(2604.105)_{10} = (?)_{16}$ 
  - (A) A2C.69
- (B) A2C.1BE
- (C) A2C.1AE
- (D) A2C.1CE
- 17. Simplified expression of  $Y = A + \overline{A} B$ is
  - (A) A + B
- (B)  $\bar{A} + B$
- (C) AB .
- (D)  $A + \overline{B}$
- 18. The output Y for the logic circuit shown in the figure is




- (A)  $\bar{A} + \bar{B}$
- (B)  $\bar{A}\bar{B}$
- (C) AB
- (D)  $A + \overline{B}$

- The mass in mechanical system is analogous to \_\_\_\_\_ in FI analogous system.
  - (A) Capacitance
- (B) Resistance
- (C) Inductance
- (D) Flux
- 20. The system with characteristic equation

$$s^4 + 3s^3 + 6s^2 + 2s + 3 = 0$$
 is

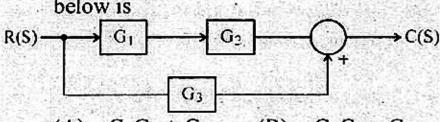- (A) Unstable
- (B) Marginally stable
- (C) Oscillating
- (D) Absolutely stable
- 21. Gain margin is a factor by which system gain can be increased to drive it to verge of
  - (A) stability
  - (B) instability
  - (C) oscillating
  - (D) initial damping
- 22. The maximum overshoot of a 2<sup>nd</sup> order system subject to unit step input can be reduced by
  - (A) reducing damping frequency
  - (B) reducing damping factor
  - (C) increasing damping factor
  - (D) increasing damping frequency
- 23. The equivalent of the system shown below is



- (A)  $G_1G_2 + G_3$
- (B)  $G_1G_2 G_3$
- (C)  $\frac{G_1G_2}{1 G_1G_2G}$
- (D)  $\frac{1}{1 + G_1 G_2 G}$

24. The corner frequency for the system with GH(s) =  $\frac{30}{s(s+2)(s^2+2s+2)}$ 

are


- (A) 0.5 r/sec, 0.707 r/sec
- (B) 0.5 r/sec, 1.41 rad/sec
- (C) 2 r/sec, 0.707 r/sec
- (D) 2 r/sec, 1.41 rad/sec
- 25. Size of on-chip ROM for 8051 microcontroller is
  - (A) 4 kbytes
- (B) 16 kbytes
- (C) 128 bytes
- (D) 64 kbytes
- 26. Instruction to mask the LSB of 'A' register content in 8051 is
  - (A) ANL A, #7F
  - (B) ANL A, # FD
  - (C) ANL A, # FE
  - (D) ANL A, #FF
- 27. Calculate the size of instruction: MOV A, R<sub>2</sub> in 8051
  - (A) 4 bytes
- (B) 3 bytes
- (C) 2 bytes
- (D) 1 byte
- 28. PSW value for selecting Bank-3 in 8051 is
  - (A) 08 H
- (B) 18 H
- (C) 00H
- (D) 01H
- 29. The value of TMOD register to operate Timer-1 in Mode-2 is
  - (A) 02 H
- (B) 40 H
- (C) 20 H
- (D) 10 H
- 30. In 8051, the highest priority interrupt
  - (A) INT 1
- (B) TF 1
- (C) TF 0
- (D) INT 0

Space For Rough Work

EE,

 $(15 \times 2 = 30)$ 

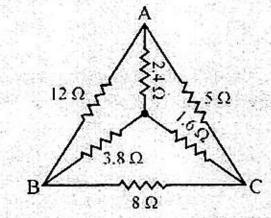- 31. For  $u = log \left[ \frac{x^3 + y^3}{xy^4} \right]$ ,  $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y}$  is equal to
  - (A) 1
- (B) 1
- (C) 2
- (D) -2
- 32. Eigen values of  $\begin{bmatrix} 1 & 1 & 3 \\ 1 & 5 & 1 \\ 3 & 1 & 1 \end{bmatrix}$  are
  - (A) 2, 2, 4
- (B) 1, 2, 5
- (C) 0, 1, 6
- (D) -2, 3, 6
- 33. Solution of  $x^2y'' 3xy' + 4y = 0$  is
  - (A)  $(C_1 + C_2 x)e^{2x}$
  - (B)  $(C_1 + C_2 x)e^{-2x}$
  - (C)  $(C_1 + C_2 \log x)x^2$
  - (D)  $(C_1 + C_2 \log x) e^{2x}$
- 34. Find the equivalent resistance between B and C.




- $(A) \cdot 1\Omega$
- (B) 2.709 Ω
- (C) 5.7 Ω
- (D) 10 Ω

- 35. A series RLC circuit has R = 10 Ω, L = 0.1 H, C = 100 μF and is connected across 200 V, variable frequency source. Find resonant frequency and voltage drop across C & L at this frequency.
  - (A) 100 Hz, 300 V
  - (B) 500 Hz, 600 V
  - (C) 50.34 Hz, 632 V
  - (D) 1000 Hz, 600 V
- 36. Expression for field intensity E for an infinite length of wire is given at (linear charge density ρ<sub>i</sub>C/m)
  - (A)  $\rho/2\pi\epsilon$
- (B)  $\rho_i/2\pi$
- (C)  $\rho/(2\pi\epsilon h)$
- (D)  $\rho/2$
- 37. In a JKFF,  $J = \overline{Q}$  and K = 1. Assuming the FF was initially cleared and then clocked for 6 pulses, the sequence at the Q output will be
  - (A) 010000
- (B) 010010
- (C) 010101
- (D) 011001
- 38. A counter with 10FFs is initialized to 0. What will be the count after 2060 pulses?
  - (A) 000 000 1100
  - (B) 000 001 1100
  - (C) 000 001 1000
  - (D) 000 000 1110



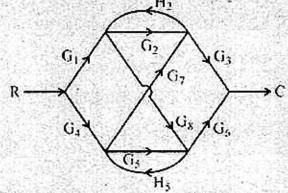- 39. A crystal has the following parameters L = 3H,  $C_S = 0.05$  pF, R = 2 k $\Omega$  and  $C_M = 10$  pF. Calculate the parallel resonant frequency of the crystal.
  - (A) 410.9 kHz
- (B) 411.7 kHz
- (C) 510.9 kHz
- (D) 511.7 kHz
- 40. The number of forward path in the following signal flow graph is



- (A) 4 (C) 2
- (B) 6 (D) 8
- 41. A system with GH(s) =  $\frac{8}{s(s^2 + 2s + 4)}$ 
  - oscillates at a frequency of
    - (A) 6 r/sec
- (B) 4 r/sec
- (C) 2 r/sec
- (D) 5 r/sec
- 42. State space representation of a system with equation
  y"' + 6y" + 10y' + 5y = u is x' = Ax +
  - y''' + 6y'' + 10y' + 5y = u is x' = Ax + BuThe matrix A is
  - (A)  $\begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -5 & -10 & -6 \end{bmatrix}$ (B)  $\begin{bmatrix} 0 & 0 & 1 \\ 0 & 0 & 1 \\ -5 & -10 & -6 \end{bmatrix}$ (C)  $\begin{bmatrix} 0 & 1 & 0 \\ 1 & 0 & 0 \\ -6 & -10 & -5 \end{bmatrix}$   $\begin{bmatrix} 1 & 0 & 0 \end{bmatrix}$

-5 -10

43. Find the content of register 'A' after executing the following set of instructions:

CLR A

ORL A, # 99H

RR A

- (A) 66 H
- (B) 99 H
- (C) 33 H
- (D) CC H
- 44. What is the content of R<sub>3</sub> after executing the following instructions:

MOV A, #220

CPL A

 $MOV R_3, A$ 

- (A) 43 H
- (B) 23 H
- (C) 13 H
- (D) 33 H
- 45. For an 8051 system of 11.0592 MHz, find the time delay for the following code:

MOV R<sub>1</sub>, #200

UP: NOP

NOP-

DJNZ  $R_1$ , UP

- (A) 869 µs
- (B) 742 μs
- (C) 272 μs
- (D) 421µs

Space For Rough Work

(D)

### (E & E : ELECTRICAL AND ELECTRONICS ENGINEERING)

#### PART - B

## (SECTION - I)

Each question carries one mark.


 $(20\times1=20)$ 

<b>46. 47.</b>	Which of the following DC generators cannot build up on open circuit?  (A) Series (B) Shunt  (C) Long Shunt (D) Short Shunt  If field resistance of DC shunt	<ul><li>51. Open circuit test on a transformer is always made with winding open circuited.</li><li>(A) low voltage</li></ul>
	generator is increased beyond its critical value, then the generator	(B) high voltage (C) low voltage or high voltage
	<ul> <li>(A) output voltage will exceed name plate rating.</li> <li>(B) fails to build up.</li> <li>(C) may burn out if loaded to its name plate rating.</li> </ul>	(D) none of these  52. When primary of transformer is connected to DC supply, then
	(D) power output may exceed name	(A) primary draws smaller current
48.	plate details.  The effect of increasing air gap in induction motor will result in increase	(B) primary leakage reactance is increased (C) core loss increases
	of (A) power factor (B) speed	(D) primary winding may burn out
	(C) air gap flux (D) magnetizing current	53. The no-load input of transformer is practically equal to
49.	The condition for maximum torque under running condition of Induction motor is	(A) copper loss (B) eddy loss (C) iron loss
	(A) $R_2 = SX_2$ (B) $X_2 = SR_2$ (C) $R_2 = X_2/S$ (D) $R_2 = X_2$	(D) stray loss
50.	For eliminating 7th harmonics from emf wave the armature of alternator should be having fractional pitch of	54. A 150 kVA, 2200/110 V transformer has iron loss of 1 kW. The maximum efficiency occurs when copper loss is  (A) 1.5 kW (B) 2 kW
	(A) 2/3 (B) 5/6 (C) 7/8 (D) 6/7	(C) 0.5 kW (D) 1 kW



- Saving of copper in autotransformer is times the weight of copper required for 2 winding transformer.
  - (A) K
- (B) 1 K
- (C) 2K
- (D) 2(1-K)
- The thermal efficiency of a steam power station is about
  - (A) 28%
- 69% (B)
- (C) 80%
- (D) 75%
- The load factor (L.F.), maximum demand (M.D.), average load (A.L.) are related as
  - (A) L.F. =  $\frac{A.L}{M.D.}$
  - (B)  $L.F. = A.L. \times M.D.$
  - (C) L.F. =  $\frac{M.D.}{A.L.}$
  - (D) L.F. = M.D.
- The correct relation in the following is
  - (A)  $kVAR = kW \sin \phi$
  - (B)  $kVAR = kW \tan \phi$
  - $kVAR = kW \cos \phi$
  - (D) None
- Cables and lines are mostly
  - (A) Inductive
- (B) Capacitive
- (C) Resistive
- (D) None
- The short circuit kVA is maximum when fault occurs
  - (A) near the generator
  - (B) at the end of transmission line
  - (C) in the middle of transmission line
  - (D) all of the above

- The correct relation for the operator a 61.  $= 1 | 120^{\circ}$  is
  - (A)  $1 + a + a^2 = 0$  (B)  $a + a^2 = 1$
  - (C)  $1 + a^3 = 0$  (D)  $a^2 + a^3 = 1$
- The safest mode of triggering SCR is 62.
  - (A) high voltage across A-K
  - (B) dv/dt exceeds the limit
  - (C) gate drive
  - (D) thermal effect
- The voltage blocking capability of a 63. switch is increased by
  - (A) heavily doped n-drift layer
  - (B) lightly doped n drift layer
  - (C) area of cross-section of layers
  - (D) inserting capacitor across switch
- Reverse recovery time of a diode is 64. 3 µs and the rate of fall of the diode current is  $di/dt = 30 \text{ A/}\mu\text{s,then peak}$ reverse current IRR is
  - (A) 10 A
- (B) 0.1 A
- (C) 9 A
- (D) 90 A
- Given supply voltage  $V_s = 10 \text{ V}$ , the 65. average value output voltage for the waveform shown is

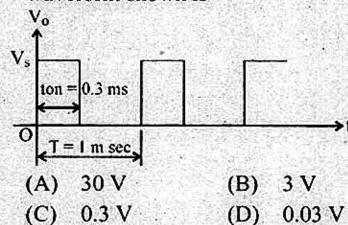

- 66. A 220 V shunt motor develops a torque of 54 Nm at armature current of 10 A. The torque developed at armature current of 20 A is
  - (A) 54 Nm
- (B) 81 Nm
- (C) 108 Nm
- (D) · 27 Nm
- 67. A 6-pole, 50 Hz, 3φ induction motor is running at 950 rpm and has rotor copper loss of 5 kW. Its rotor input is
  - (A) 100 kW
- (B) 10 kW
- (C) 95 kW
- (D) 5.3 kW
- 68. A 3φ, 4-pole, 440 V induction motor has synchronous speed of 1500 rpm and has slip of 5%. The frequency of rotor emf is
  - (A) 4 Hz
- (B) 2 Hz
- (C) 3 Hz
- (D) 5 Hz.
- 69. A transformer has flux density of 1.6 tesla, frequency of 50 Hz, area of iron in core= 0.0707 m<sup>2</sup>. The emf per turn induced will be
  - (A) 10.65 V
- (B) 25.1 V
- (C) 7.95 V
- (D) 106.56 V
- 70. A transformer delivering 100 kW at UPF has copper loss of 2 kW at this load. The maximum efficiency will be
  - (A) 94.56%
- (B) 96.15%
- (C) 98.04%
- (D) 99.1%
- 71. A 50 kVA transformer has iron loss of 500 W, full load copper loss of 800 W. The efficiency at full load, 0.8 pF lag is
  - (A) 92%
- (B) 89.56%
- (C) 96.85%
- (D) 95.82%

- 72. A workshop is consuming 500 kW at 0.707 pF lagging. A synchronous motor is connected to improve the P.F. to 0.95 lagging. The leading reactive power supplied by the synchronous motor is
  - (A) 250 kVAR
- (B) 228 kVAR
- (C) 150 kVAR
- (D) 336 kVAR
- 73. The currents in a  $3\phi$  unbalanced system are  $\overrightarrow{IR} = (12 + j6)A$ ;  $\overrightarrow{IY} = (12 j12)A$ ;  $\overrightarrow{IB} = (-15 + j10)A$ . The phase sequence is RYB. The zero phase sequence component in R phase is
  - (A) (1.5 + j2.3)A
  - (B) (3 + j 1.33)A
  - (C) (2.8 + j 6.7)A
  - (D) (1.5 + j 0.15)A
- 74. A UJT triggering circuit is connected across a 20 V zener. The valley and peak voltages are 1 V & 15 V respectively. The intrinsic stand off ratio is 0.75. It operates at a frequency of 1200 Hz. Find the charging capacitance of R = 5.6 kΩ.
  - (A) 10.7 μF
- (B)  $1.07 \, \mu F$
- (C)  $0.107 \, \mu F$
- (D)  $0.0107 \, \mu F$
- 75. A plywood having capacitance of 14.76 pF is subjected to dielectric heating at 20 MHz. The power observed is 400 W and  $\delta = 0.05$ . The voltage required for heating is
  - (A) 1076 V
- (B) 2076 V
- (C) · 3076 V
- (D) 8076 V

11

# (E & C AND TC : ELECTRONICS AND COMMUNICATION ENGINEERING AND TELECOMMUNICATION ENGINEERING)

#### PART - B


#### (SECTION-I)

#### Each question carries one mark.

 $(20\times 1=20)$ 

- 46. The minimum number of transistor required to implement 2 input X-OR Gate in CMOS technology:
  - (A) 2
  - (B) 4
  - (C) 6
  - (D) 8
- 47. The Gate capacitance (C<sub>g</sub>) of a MOSFET is given by
  - (A)  $C_g = C_o L.W.$
  - (B)  $C_g = C_o \frac{W}{L}$
  - (C)  $C_g = C_o \frac{L}{W}$
  - (D)  $C_g = \frac{W.L}{C_o}$
- 48. In Embedded systems the initialization routine is often referred as
  - (A) Initial program
  - (B) Bootstrap program.
  - (C) Reboot program
  - (D) Starting program

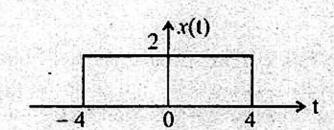- 49. The input and output of a continuous time system are represented by x(t) and y(t) respectively. Which of the following corresponds to a causal system?
  - (A) y(t) = (t+4)x(t-1)
  - (B) y(t) = (t+5)x(t+1)
  - (C) y(t) = (t-4)x(t+2)
  - (D) y(t) = x(t-3) + x(t+2)
- 50. The average power (P) and energy (E) of the signal x(t) shown in figure below is



- (A) P = 16 W, E = 32 J
- (B) P = 0, E = 32 J
- (C) P = 0 E = 16.
- (D)  $P = \infty$ , E = 48 J

- 51. The number of stages required to compute 512-point DFT using Radix-2 DIF FFT algorithm is
  - (A) 9
  - (B) 8
  - (C) 7
  - (D) 6
- 52. Four independent messages have bandwidth of 100 Hz, 100 Hz, 200 Hz and 400 Hz respectively. Each is sampled at Nyquist rate and samples are Time Division Multiplexed (TDM) and transmitted. The transmitted sample rate (in Hz) is
  - (A) 800
  - (B) 1600
  - (C) 400
  - (D) 3200
- 53. In PCM, if the number of quantization levels is increased from 4 to 64, then the bandwidth requirement will approximately equal to
  - (A) 3 times
  - (B) 4 times
  - (C) 2 times
  - (D) 16 times

- 54. A modulated signal is given by  $\delta(t) = e^{-at} \cos[(w_c + \Delta w)t]u(t)$  where a,  $w_c$  and  $\Delta w$  are positive constants and  $w_c >> \Delta w$  the complex envelope of  $\delta(t)$  is given by
  - (A)  $e^{-at} e^{-j(w_c + \Delta w)t.u(t)}$
  - (B)  $e^{-at} e^{-j \Delta wt. u(t)}$
  - (C)  $e^{-j \Delta w t u(t)}$
  - (D)  $e^{j(w_c + \Delta w)t}$
- 55. The thermal noise power contribution is limited only by the \_\_\_\_\_ of the circuit.
  - (A) Bandwidth
  - (B) Boltzman's constant
  - (C) Resistor
  - (D) Temperature
- 56. Directivity of an Isotropic radiator is
  - (A) 0
- (B) 1
- (C) 2
- (D) 3
- 57. Unit of Beam area is
  - (A)  $m^2$
  - (B) degrees
  - (C) steradians
  - (D) radians



58.	VSWR of a short circuited transmission line is	62.	in phase controlled rectifiers.
	(A) 0 (B) 1		(A) Line
	(C) 10 (D) ∞		(B) Load
			(C) Forced
70			(D) External-pulse
59.	Dominant mode of wave propagation in a circular waveguide is		
	(A) TE <sub>00</sub> (B) TE <sub>01</sub>	63.	Instruction to perform 2's complement of a source in 8086 is
	(C) TE <sub>10</sub> (D) TE <sub>11</sub>		(A) CPL
			(B) NOT
60. In an SCR, the angle of conduction can be changed by changing			(C) NEG
		(D) CMC	
	(A) Anode voltage	64.	Which of the following is not a data
7/6 1	(B) Forward current rating		transfer instruction in 8086?
	(C) Anode current		(A) DAA
	(D) Gate current		(B) MOV
			(C) POP
			(D) PUSH
61.	1. Which power device is most suitable for high frequency (> 100 kHz) switching application?		IN BSR mode, only PORT-C can be
	(A) Power MOSFET		used to
			(A) reset individual port bits
	(B) BJT		(B) set and reset individual port bits
	(C) Schottky diode		(C) set individual port bits
	(D) IGBT		(D) None of the above



- 66. The drain of an n-channel MOSFET is shorted to the gate so that  $V_{GS} = V_{DS}$ . The threshold Voltage  $(V_T)$  of MOSFET is 1 V. If the drain current  $I_D$  is 1 mA for  $V_{GS} = 2V$ , then for  $V_{GS} = 3V I_P$  is
  - (A) 2 mA
- (B) 3 mA
- (C) 9 mA
- (D) 4 mA
- 67. A depletion type N-channel MOSFET in biased in its region for use as a voltage controlled resistor. Assume threshold voltage  $V_{Th} = 0.5 \text{ V}$ ,  $V_{GS} = 2.0 \text{ V}$ ,  $V_{DS} = 5 \text{V}$ , W/L = 100,  $C_{ox} = 10^{-8} \text{F/cm}^2$  and  $\mu_n = 800 \text{ cm}^2/\text{V-s}$ . The value of the resistance of the voltage controller resistor (in Ω) is
  - (A)  $100 \Omega$
- (B)  $200 \Omega$
- (C)  $300 \Omega$
- (D) 500 Ω

- 68. Two discrete time LTI systems with impulse responses h<sub>1</sub>(n) = δ(n 2) and h<sub>2</sub>(n) = δ(n 3) are connected in cascade. The overall impulse response of the cascaded system is
  - (A)  $\delta(n+1)$
  - (B)  $\delta(n-2) + \delta(n+3)$
  - (C)  $\delta(n-2) \cdot \delta(n-3)$
  - (D)  $\delta(n-5)$
- 69. Fourier transform of the signal  $x(t) = e^{-t}u(t)$  is  $\frac{1}{1+jw}$ , then the Fourier transform of the signal x(t) + x(-t) is
  - (A)  $\frac{j 2w}{1 + w^2}$
  - (B)  $\frac{jw}{1+w^2}$
  - (C)  $\frac{2}{1+w^2}$
  - (D)  $\frac{2w}{1+w^2}$

EE

- 70. The maximum power efficiency of an AM Modulation is
  - (A) 25%
  - (B) 50%
  - (C) 75%
  - (D) 100%.
- 71. A communication channel with AWGN, has a bandwidth of 4 kHz and SNR of 15. Its channel capacity is
  - (A) 1.6 kbps
  - (B) 16 kbps
  - (C) 32 kbps
  - (D) 256 kbps
- 72. Find the HPBW of an antenna whose E-field pattern varies as  $1 + \cos \theta$ .
  - (A) 113°
  - (B) 131°
  - (C) 311°
  - (D) 65°

- 73. A single phase voltage controller has input of 230 V and resistive load of 15 Ω. For 6 cycles 'ON' and 4 cycles 'OFF' determine RMS output voltage.
  - (A) 189 V
- (B) 260 V
- (C) 156 V
- (D) 178 V
- 74. In 8086, if AL = 43 H and BL = 28 H, what will be the content of accumulator after executing the following:

ADD AL, BL

DAA

- (A) 51 H
- (B) 71 H
- (C) 81 H
- (D) 61 H
- 75. In 8086, if CS = 538A H and IP = 1234 H, calculate the 20-bit physical address.
  - (A) 54BD4 H
  - (B) 54AE4 H
  - (C) 65BE0 H
  - (D) 54AD4 H

#### (BME& ME: BIO-MEDICAL ENGINEERING & MEDICAL ELECTRONICS)

#### PART - B

#### (SECTION - I)

#### Each question carries one mark.

 $(20\times1=20)$ 

- 46. The most widely used lossless image compression format on the internet is
  - (A) JPG
- (B) PNG
- (C) GIF
- (D) MPG
- 47. A system is said to be defined as non-causal, when
  - (A) the output at the present depends on the input at an earlier time.
  - (B) the output at the present does not depend on the factor of time at all.
  - (C) the output at the present depends on the input at the current time.
  - (D) the output at the present depends on the input at a time instant in the future.
- 48. The discrete time system described by  $Y(n) = X(n^2)$  is
  - (A) causal, linear and time invariant
  - (B) causal, linear and time variant
  - (C) non-causal, linear and time invariant
  - (D) non-causal, linear and time variant

- 49. The spin-echo technique in MRI is developed to remove the effect of
  - (A) Motion artifacts
  - (B) Thermal Noise
  - (C) Stray electromagnetic effects
  - (D) H-field in homogeneity
- 50. Pacemaker used for patients having permanent heart block is
  - (A) Atrial triggered pacemaker
  - (B) Bifocal demand pacemaker
  - (C) R-wave triggered pacemaker
  - (D) Fixed rate pacemaker
- 51. The pacemaker is characterized by the code VDD. The first letter V indicates
  - (A) Ventricle paced
  - (B) Ventricle sensed
  - (C) Ventricle triggered
  - (D) Ventricle inhibited



-	D 11 1 1 1					
52.	Radiographic	grids	are	made	1110	of
200000000000000000000000000000000000000	O	C			1-	***

- (A) Yittrium tantalate
- (B) Phosphor
- (C) Calcium
- (D) Lead
- 53. In X-ray film processing, amplification of latent image takes place during
  - (A) Development
  - (B) Replenishment
  - (C) Fixing
  - (D) Washing
- 54. Evaluation of the Grid performance is based on
  - (A) Grid ratio
  - (B) Grid pattern
  - (C) Grid thickness
  - (D) Bulky factor
- 55. In Sonography, a picture of a slice of tissue is produced by
  - (A) A-mode scanning
  - (B) B-mode scanning
  - (C) C-mode scanning
  - (D) M-mode scanning

- 56. Electrodes used for EMG signals is
  - (A) Surface electrode
  - (B) Ring electrode
  - (C) Suction electrode
  - (D) Needle electrode
- 57. A pattern of electrodes placed on the scalp in measurement of EEG is called
  - (A) Frontage
- (B) Tonage
- (C) Scalpage
- (D) Montage
- 58. Impedance pneumography is a technique for the measurement of
  - (A) Blood flow rate
  - (B) Heart rate
  - (C) Respiration rate
  - (D) Body temperature
- 59. Low energy radiation encountering the electron of an atom, setting it into vibrations at the frequency of the radiation. This phenomenon is called as
  - (A) Photo disintegration
  - (B) Photoelectric effect
  - (C) Crompton effect
  - (D) Coherent scattering



- 60. In blood pressure measurement the pressure from systolic towards diastolic is bled off in the range
  - (A) 1-2 mm Hg/s
  - (B) 2-3 mmHg/s
  - (C) 3-5 mmHg/s
  - (D) 5 10 mm Hg/s
- 61. EEG waveform obtained in the frequency range of 8 Hz to 1.3 Hz are called as
  - (A) Delta
  - (B) Theta
  - (C) Alpha
  - (D) Beta
- 62. For the measurement of ECG, the electrode placement between left arm and left leg is called
  - (A) Lead I
  - (B) Lead II
  - (C) Lead III
  - (D) Lead IV

- 63. Which of the following defines rectangular window function of length M 1?
  - (A) W(n) = 1, n = 0, 1, 2 .... M 1;0 elsewhere
  - (B) W(n) = 1, n = 0, 1, 2 ... M 1;-1 elsewhere
  - (C)  $W_n(n) = 0, n = 0, 1, 2 \dots M 1;$ 1 elsewhere
  - (D) W(n) = -1, n = 0, 1, 2, ..., M 1;0 elsewhere
- 64. In sonography the coefficient for the flat tissue is
  - (A) 0.18 dB/cm
  - (B) 0.63 dB/cm
  - (C) 0.85 dB/cm
  - (D) 1.00 dB/cm
- 65. The concurrent use of continuous RF current for cutting and coagulation is called
  - (A) Polarization
  - (B) Hemostasis
  - (C) Electrotomy
  - (D) Thermostat

#### Each question carries two marks.

 $(10 \times 2 = 20)$ 

- 66. Fourier transform of a rectangular pulse is
  - (A) Another rectangular pulse
  - (B) Triangular signal
  - (C) Sinc function
  - (D) Impulse function
- 67. IN IIR digital filter, the present output depends on
  - (A) present and previous inputs only
  - (B) present input and previous outputs only
  - (C) present input only .
  - (D) present input, previous input and output
- 68. A signal x<sub>1</sub>(t) and x<sub>2</sub>(t) constitute real and imaginary parts respectively of a complex valued x(t). What form of waveform does x(t) possess?
  - (A) Real symmetric
  - (B) Complex symmetric
  - (C) Asymmetric
  - (D) Conjugate symmetric
- 69. The decay constant for the radio nuclide having the half-life of 8.04 days is
  - (A) 0.693/day
- (B) 0.863/day
- (C) 0.804/day
- (D) 0.086/day
- 70. The convolution sum of two sequences  $X(n) = \{3, 2, 1, 2\}$  and  $h(n) = \{1, 2, 1, 2\}$ 
  - (A)  $Y(n) = \{3, 8, 8, 12, 9, 4, 4\}$
  - (B)  $Y(n) = \{3, 8, 3, 12, 9, 4, 4\}$
  - (C)  $Y(n) = \{3, 8, 8, 12, 9, 1, 4\}$
  - (D)  $Y(n) = \{3, 8, 8, 1, 9, 4, 4\}$

- 71. What is the Nyquist rate for the signal given:
  - $x(t) = \cos 2000 \pi t + 3 \sin 6000 \pi t$
  - (A) 2 kHz
- (B) 4 kHz
- (C) 12 kHz
- (D) 6 kHz
- 72. The resultant vector formed in an Einthovens triangle is for which of the Lead combination?
  - (A) I + III = II
- (B) I III = II
- (C) I + II = III
- (D) II + III = I
- 73. Calculate the maximum frequency of a Doppler-Ultrasound blood flowmeter, that has a carrier frequency of 7 MHz, a transducer angle of 45°, blood velocity of 150 cm/s and an acoustic velocity of 1500 m/s
  - (A) 1 kHz
- (B) 10 kHz
- (C) 14 kHz
- (D) 19 kHz
- 74. The convolution of f(t) with itself is

given to be  $\int_{0}^{t} f(t).dt$ , then what is f(t)?

- (A) The unit ramp function
- (B) Equal to 1
- (C) The unit step function
- (D) The unit impulse function
- 75. The Fourier transform of f(t) is F(jW), then what is the Fourier transform of f(-t)?
  - (A) F(jW)
  - (B) F(-jW)
  - (C) -F(jW)
  - (D) Complex conjugate of F(jW)

## (IT: INSTRUMENTATION TECHNOLOGY) PART - B

#### (SECTION - I)

Each question carries one mark.

 $(20\times1=20)$ 

- The difference between the measured 46. value and true value is
  - (A) Gross error
  - Relative error (B)
  - Probable error (C)
  - Absolute error
- According to Gaussian Statistical Analysis, if the confidence interval is 0.80, then the values lying outside the confidence interval are
  - (A) 1 in 5
  - (B) 1 in 10
  - 1 in 20.
  - (D) 8 in 10
- Error caused by the measurement on the physical system being tested is
  - (A) Hysteresis error
  - Random error (B)
  - Systematic error
  - Loading error (D)

- Two strain gauges are used to measure strain in cantilever. One gauge is mounted on the top of the cantilever and other is placed at the bottom. Two strain gauges form, two arms of Wheatstone's bridge. The bridge configuration is called as
  - (A) a quarter bridge
  - a half bridge (B)
  - a full bridge (C)
  - (D) a null bridge
- The function of a reference electrode 50. in a pH meter is to
  - (A) produce a constant voltage
  - provide temperature compensation (B)
  - provide a constant current (C)
  - (D) measure average pH value
- The most light sensitive transducer for 51. conversion of light into electrical power is
  - (A) Photodiode
  - (B) Solar cell
  - (C) Photovoltaic cell
  - Photo conductive cell (D)



- 52. The technique used to analyse the property of Radiation diffraction is
  - (A) Photometry
  - (B) Coulometry
  - (C) X-ray spectroscopy
  - (D) Calorimetry
- 53. Lenses used in optical filters are made up of
  - (A) Aluminium
  - (B) Gold
  - (C) Copper
  - (D) Fused silica
- 54. The wavelength calibration of a spectrophotometer can be checked by
  - (A) Aluminium filter
  - (B) Holomium oxide filter
  - (C) Beryllium filter
  - (D) Synthetic quartz filter
- 55. The dielectric layer used in interference filters of spectrophotometers is
  - (A) ZnS
  - (B)  $Ba_2Ta_2O_6$
  - (C) SiO<sub>2</sub>
  - (D) CSO<sub>4</sub>

- 56. The inverse Fourier transform of  $\delta(f)$  is
  - (A) u(t)
  - (B)
  - (C)  $\delta(t)$
  - (D)  $e^{j2\pi t}$
- 57. Which one of the following can act as an inverse transducer?
  - (A) LVDT
  - (B) Strain gauge
  - (C) Piezoelectric crystal
  - (D) Bimetal strip
- 58. The process of imitating one system with another so that the imitating systems accepts the same data, executes same programs and achieves same results as the imitated systems is known as
  - (A) Simulation
  - (B) Modification
  - (C) Translation
  - (D) Emulation
- 59. A servo motor is mainly used for
  - (A) Position control
  - (B) Velocity control
  - (C) Acceleration control
  - (D) Both velocity and acceleration control

- 60. Deuterium discharge lamp has the wavelength in the range:
  - (A) 60 90 nm
  - (B) 90 140 nm
  - (C) 160 360 nm
  - (D) 450 600 nm
- 61. The frequency range of the signal is in the range of 10<sup>15</sup> to 10<sup>17</sup> Hz. This belong to the radiation band of
  - (A) Gamma rays
  - (B) Ultraviolet rays
  - (C) X-rays
  - (D) Infra-red
- 62. Typical current used in stimulation of cardiac cells for the clinical applications of cardiac defibrillation is
  - (A) 50 200 mA
  - (B) 10-100 mA
  - (C) 0.25 35 mA
  - (D) 1 to 10 mA

- 63. OTDR is the acronym for
  - (A) Optical Time Domain Reflectometry
  - (B) Optical Transmission and Detection Ratio
  - (C) Optical Time Domain Deflection Region
  - (D) Optical Transmission and Deflection Ratio
- 64. Optical pyrometer is used to measure
  - (A) Low Pressure
  - (B) Low Temperature
  - (C) High Temperature
  - (D) High Pressure
- 65. Which one of the following quantities can be measured with the help of piezoelectric crystal?
  - (A) Acceleration
  - (B) Flow
  - (C) Temperature
  - (D) Velocity

- A 0 150 V voltmeter has accuracy of 1% of full scale reading. The voltage measured by the instrument is 75%. The limiting error is
  - (A) 1%
- (B)
- (C) 2.5%
- (D) 3%
- 67. A 1 m length wire has a resistance of 150  $\Omega$  when it is subjected to strain, its length becomes 1.01 m. measurement is conducted by a strain gauge whose gauge factor is 2. The change in resistance of the wire is
  - (A)  $0.5 \Omega$
- (B)  $1.0 \Omega$
- (C) 2.0  $\Omega$
- (D)  $3.0 \Omega$
- Experiments conducted with ultraviolet light of wavelength  $1.800 \times 10^{-5}$  cm show that electrons of maximum energy 1.51 eV are ejected from a certain metal. If Planck's constant is  $6.62 \times 10^{-27}$  erg.sec, the photoelectric threshold of the metal is about
  - (A) 3.4 eV
- (B) 4.8 eV
- (C) 5.4 eV
- (D) 5.0 eV
- A 5 channel DC to 60 Hz telemetry system uses PAM and PCM systems. For a good quality data transmission, the minimum sampling rate must be
  - (A) 300 samples/sec
  - 500 samples/sec
  - (C) 1500 samples/sec
  - 1000 samples/sec
- A system has poles at 0.01 Hz, 1 Hz and 80 Hz; zeros at 5 kHz, 100 Hz and 200 Hz. The approximate phase of the system response at 20 Hz
  - -90° (A)
- 00 (B)
- 90° (C)
- (D)  $-180^{\circ}$

- 71. The 2-transform of  $\left(\frac{1}{4}\right)^n u(-n)$  is
  - (A)  $\frac{4z}{4z-1}$   $|z| > \frac{1}{4}$
  - (B)  $\frac{4z}{4z-1}$   $|z| < \frac{1}{4}$
  - (C)  $\frac{1}{1-4z}$   $|z| > \frac{1}{4}$
  - (D)  $\frac{1}{1-47}$   $|z| < \frac{1}{4}$
- The z-transform of  $\delta(n+k)$ , k > 0 is

  - (A)  $z^{-k}, z \neq 0$  (B)  $z^{k}, z \neq 0$
  - (C)  $z^{-k}$ ,  $a \parallel z$  (D)  $z^{k}$ ,  $a \parallel z$
- A PD controller is used to compensate the system. Compared to: uncompensated system, the compensated system has
  - (A) a higher type number
  - (B) a reduced dumping
  - higher noise amplification (C)
  - larger transient overshoots
- 74. The value of  $\int \sin t \cdot \delta(t \pi/4)$  dtis

- The minimum number of delay 75. elements required realizing a digital filter with a transfer function
  - $1 + az^{-1} + bz^{-2}$  $H(z) = \frac{1}{1 + cz^{-1} + dz^{-2} + ez^{-3}}$
  - (A)
- (B) 3
- (C)
- (D) 5

